
1.25 GHZ FULLY INTEGRATED DC-DC CONVERTER USING ELECTROMAGNETICALLY COUPLED CLASS-D LC OSCILLATORS

[Ph.D student update Work presented at ISSCC 2021]

Alessandro Novello
Ph.D Student at ETH Zurich

alessandro.novello@iis.ee.ethz.ch

February 25, 2021

About SSCS

SSCS Education Material:

- ✓ **SSCS Resource Center – free for SSCS members – includes short courses, tutorials, CONFedu series, lecture series, past webinars**
- ✓ **Distinguished Lecture Program: exclusive to SSCS members**
- ✓ **Webinars: free access to all SSCS members**
- ✓ **Membership is only \$22 for 2018**
- ✓ **\$11 for students**
- ✓ **Join at www.sscs.org**

<https://resourcecenter.sscs.ieee.org/>

About Alessandro Novello





ETH zürich

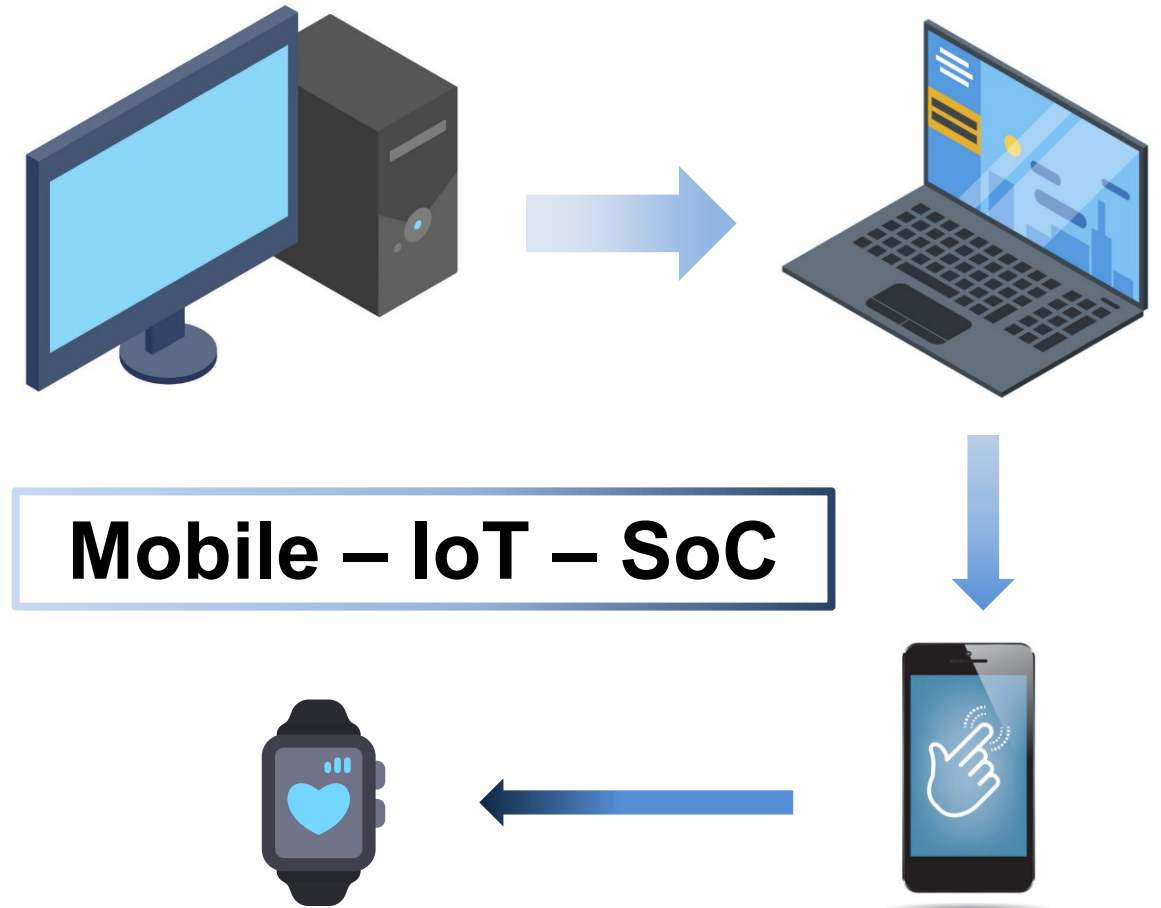 
1. 2016, B.S degree in electronic engineering from Polytechnic University of Turin
2. 2018, M.S degrees in Micro and Nanotechnologies for Integrated Systems (EPFL/Poly Torino/INP Grenoble)
3. Currently pursuing Ph.D in the Energy Efficient Circuits and IoT Systems at ETH. Main research interests include Power Management IC design and Energy Harvesting circuits for ultra-low power
4. Distinguished contribution to SSCs conferences in 2020 and 2021

Background and Motivations

Fully integrated DC-DC converter publications




Conventional Switched Capacitor (SC)

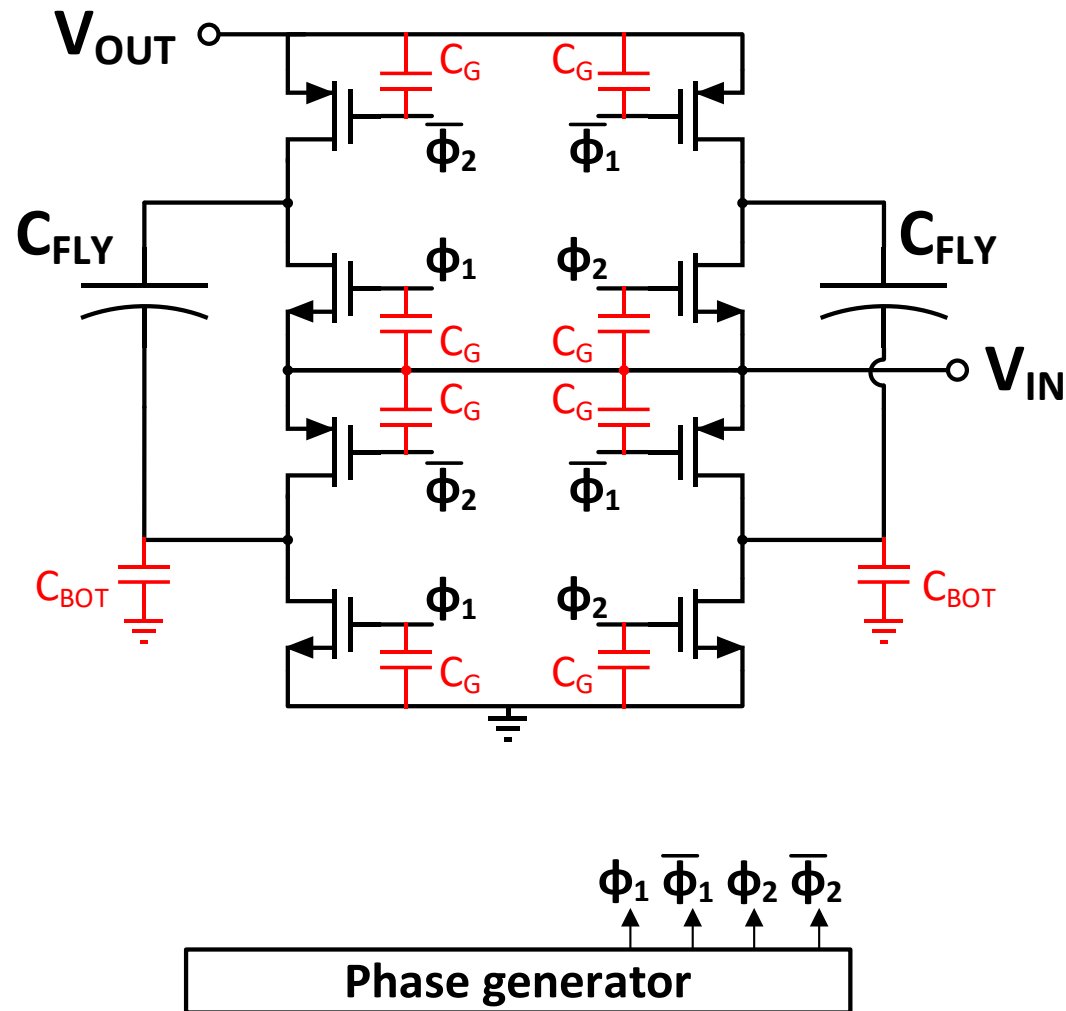

- ☹ C_{BOT} switching loss
- ☹ C_G switching loss
- ☹ Low power density
- ☹ Auxiliary circuitry
- ☹ Large load capacitor


Resonant Drain SC

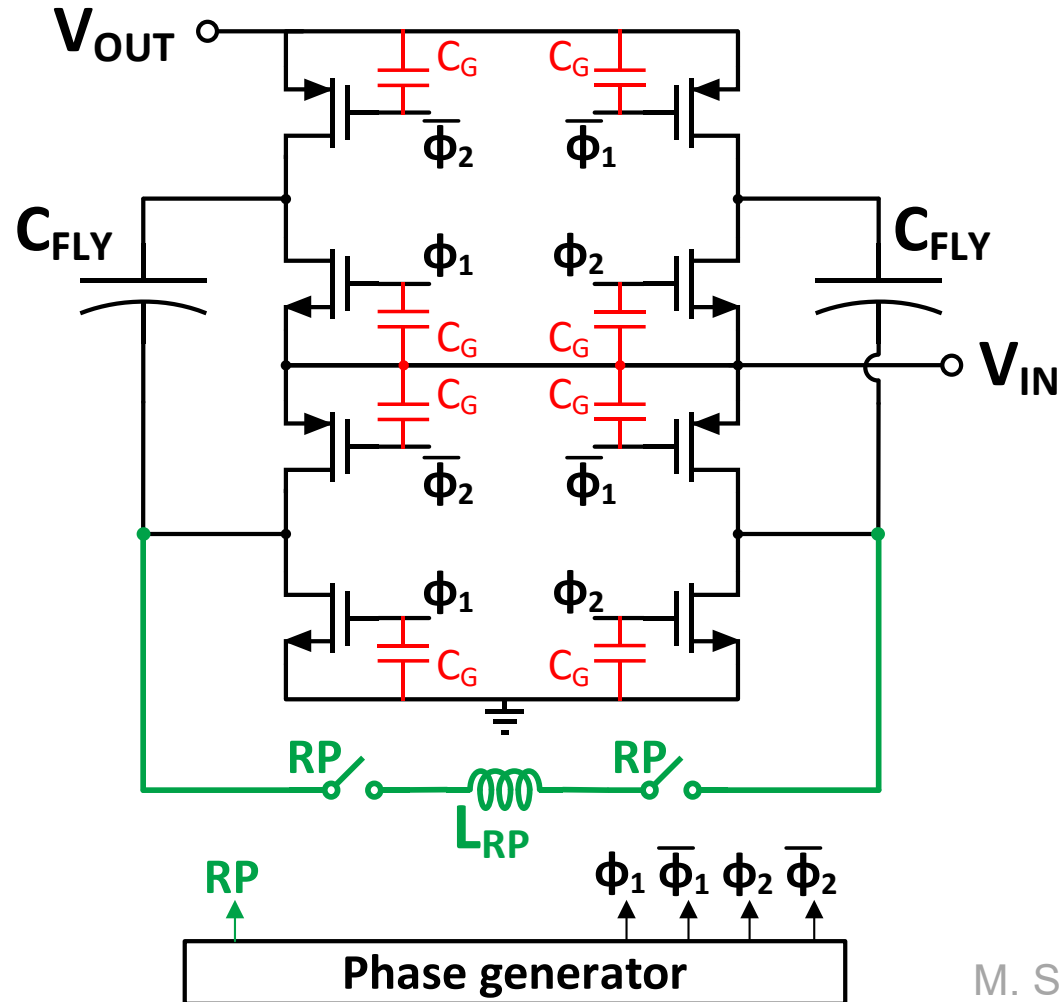

- 😊 C_{BOT} switching loss
- ☹️ C_G switching loss
- ☹️ Low power density
- ☹️ Auxiliary circuitry
- ☹️ Large load capacitor

M. Seeman, PhD dissertation, 2009


Resonant Gate SC

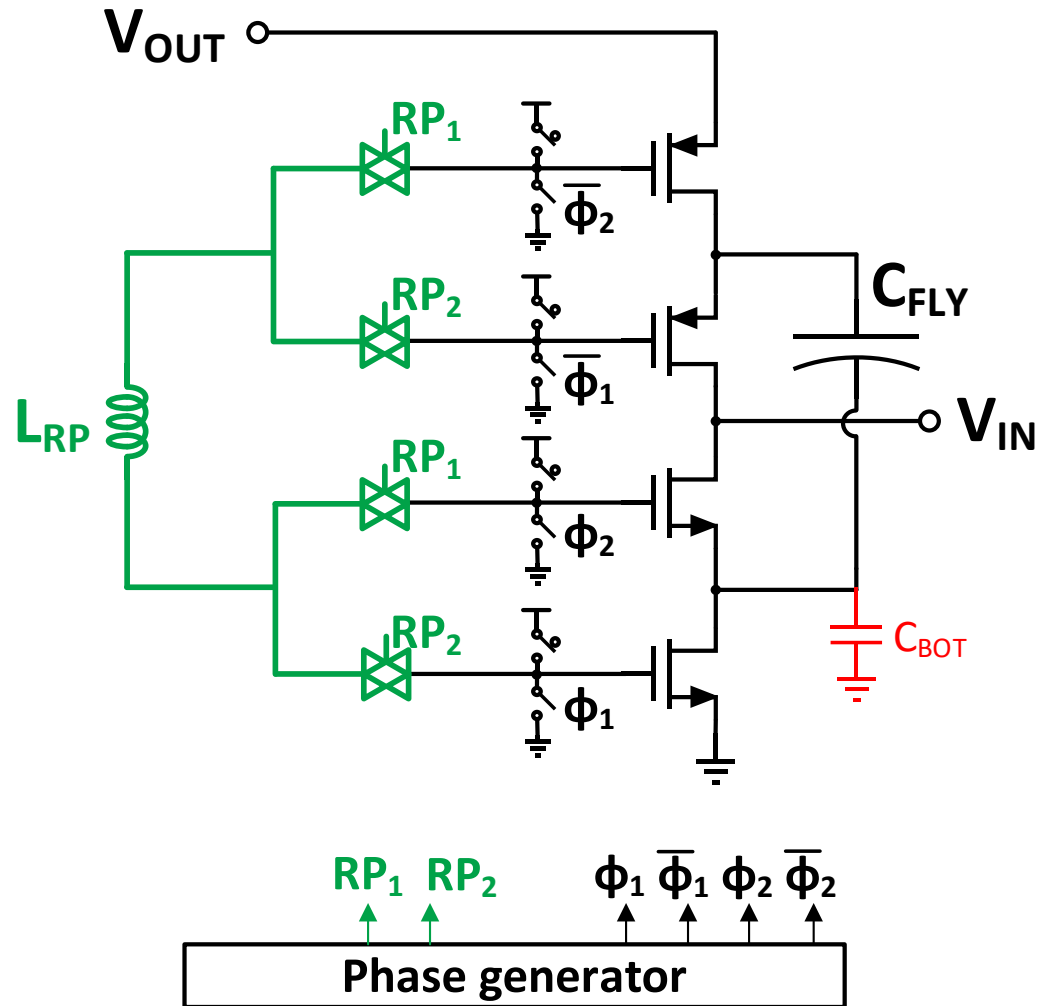

- ☹️ C_{BOT} switching loss
- ☺️ C_G switching loss
- ☹️ Low power density
- ☹️ Auxiliary circuitry
- ☹️ Large load capacitor

M. Abdelfattah, ISSCC18'


Hybrid-Resonant SC

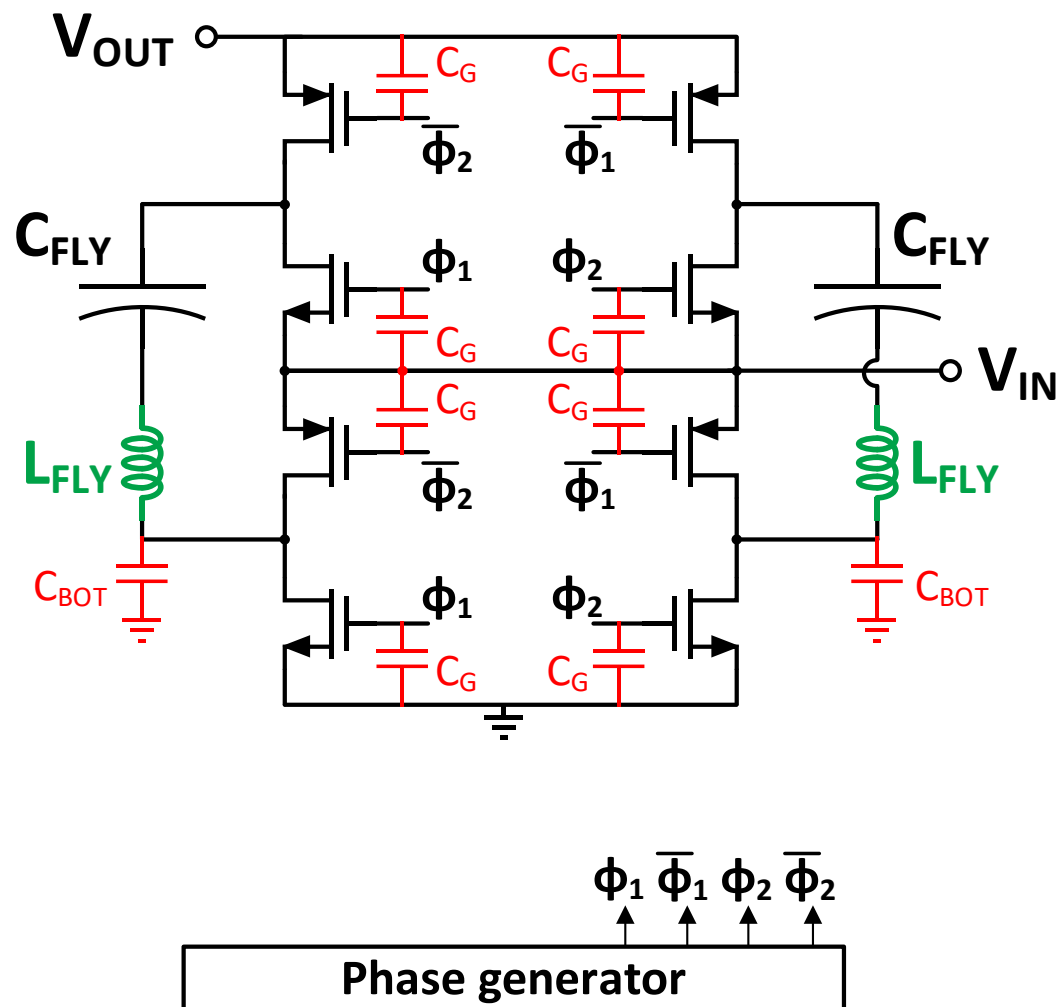

- ☹️ C_{BOT} switching loss
- ☹️ C_G switching loss
- 😊 **High power density**
- ☹️ Auxiliary circuitry
- ☹️ Large load capacitor



K. Kesarwani, ISSCC14'

Proposed EM coupled class-D LC 1:2

 



- ☺ C_{BOT} switching loss
- ☺ C_G switching loss
- ☺ High power density
- ☺ No auxiliary circuitry
- ☺ No large load capacitor

Operating Principles

  



- V_{IN} starts the oscillation on the nodes V_A and V_C

Operating Principles

  



- V_B and V_D follow V_A and V_C thanks to the vertical electric coupling

Operating Principles

 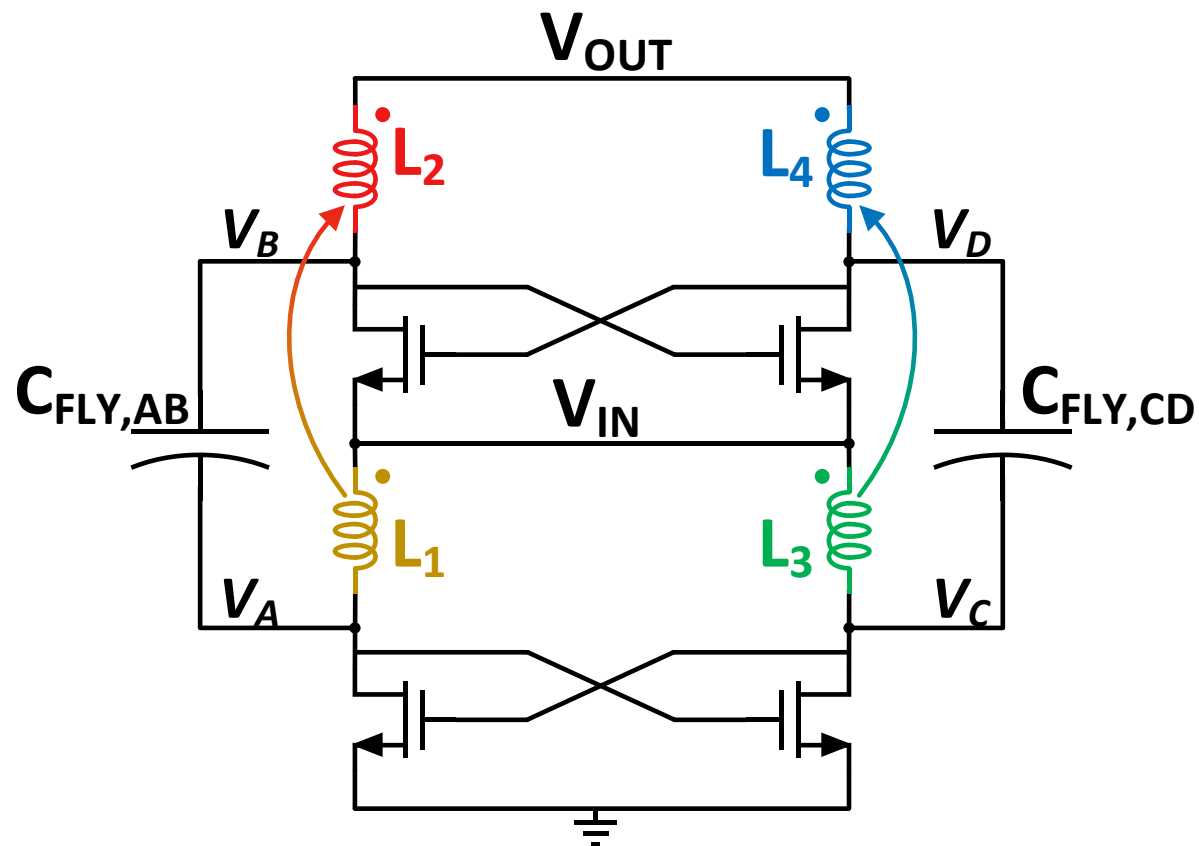



- Vertical magnetic coupling introduces current coupling
- V_{OUT} is built in between L_2 and L_4

Operating Principles

  

- **I_{LOAD} = 0**: inductor currents oscillating close to 0



Operating Principles

  

- $I_{LOAD} > 0$: inductor currents DC component shifted

Operating Principles



Phase Φ_{1A}

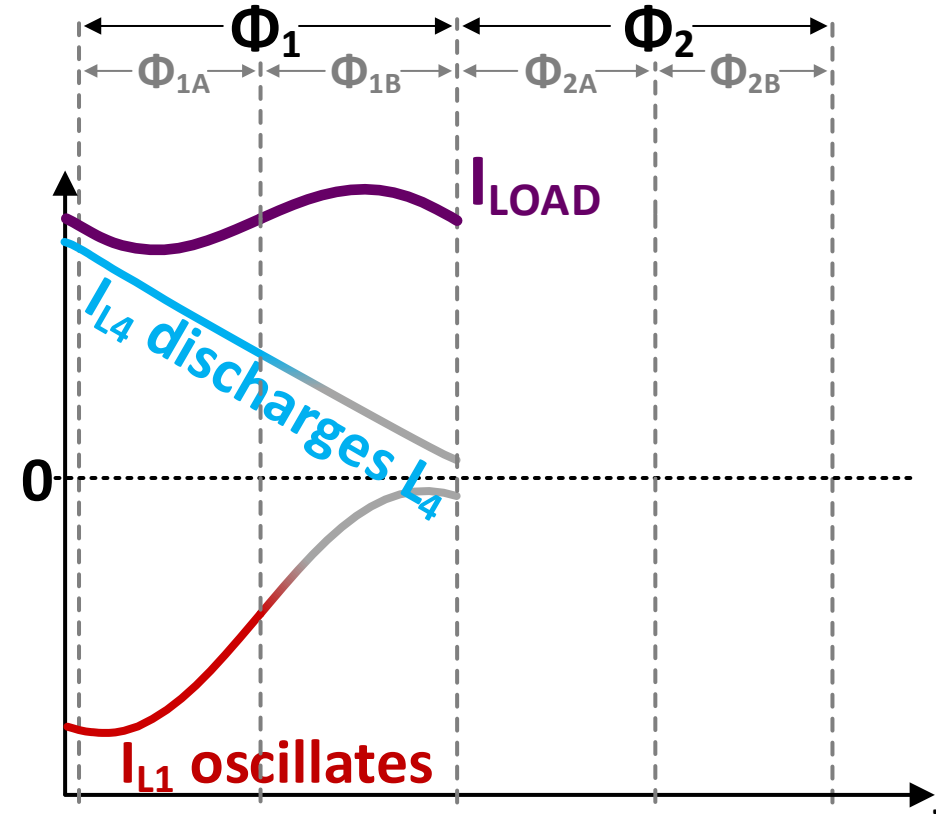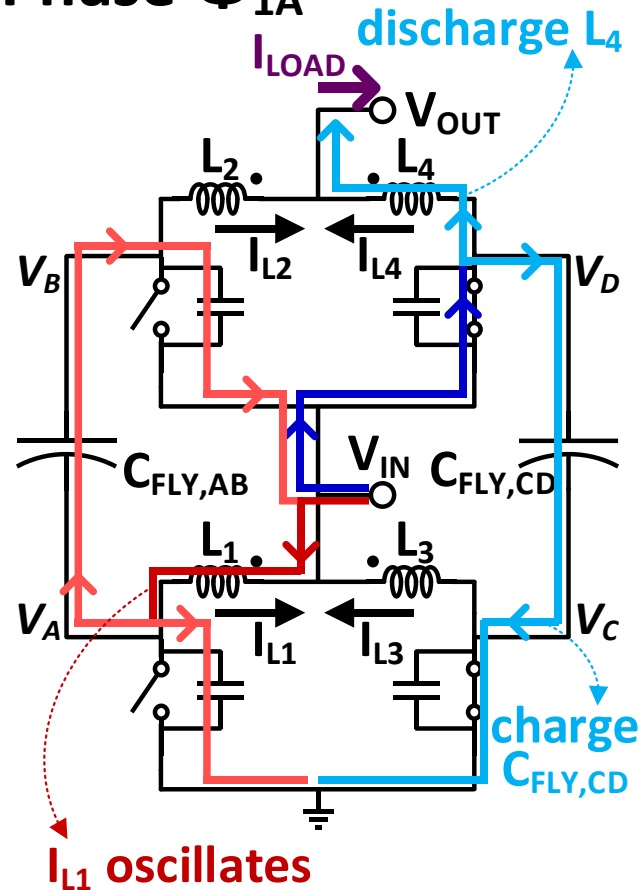

- Φ_{1A} : L_1 energizing both oscillators, L_4 delivering I_{LOAD}

Operating Principles



Phase Φ_{1B}

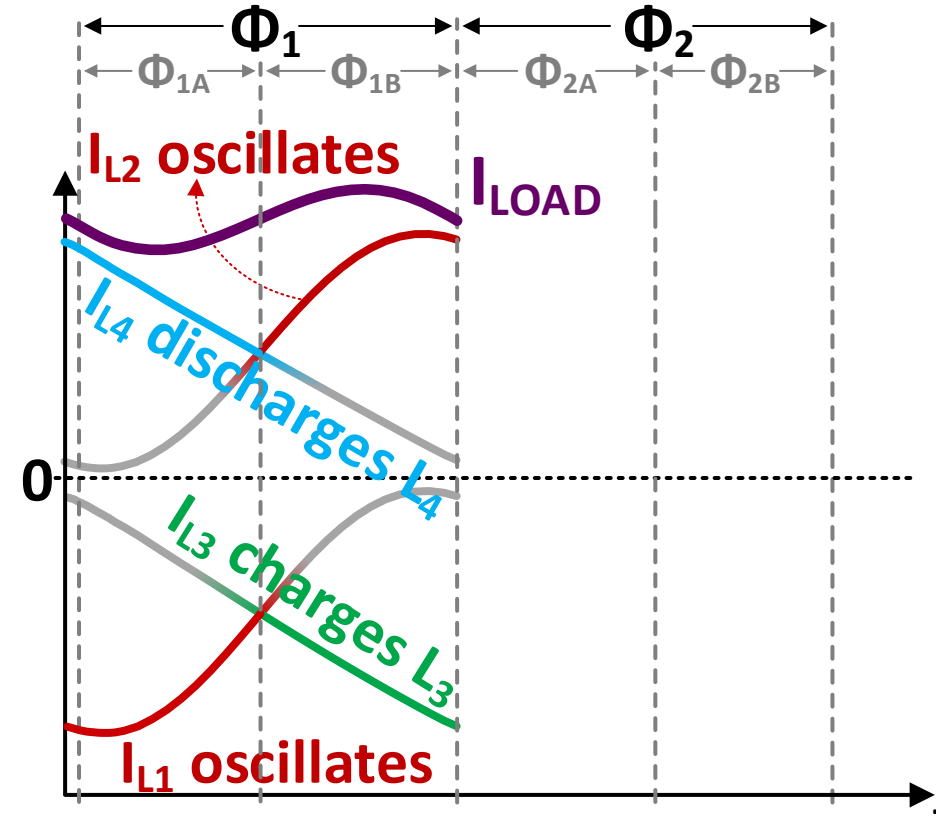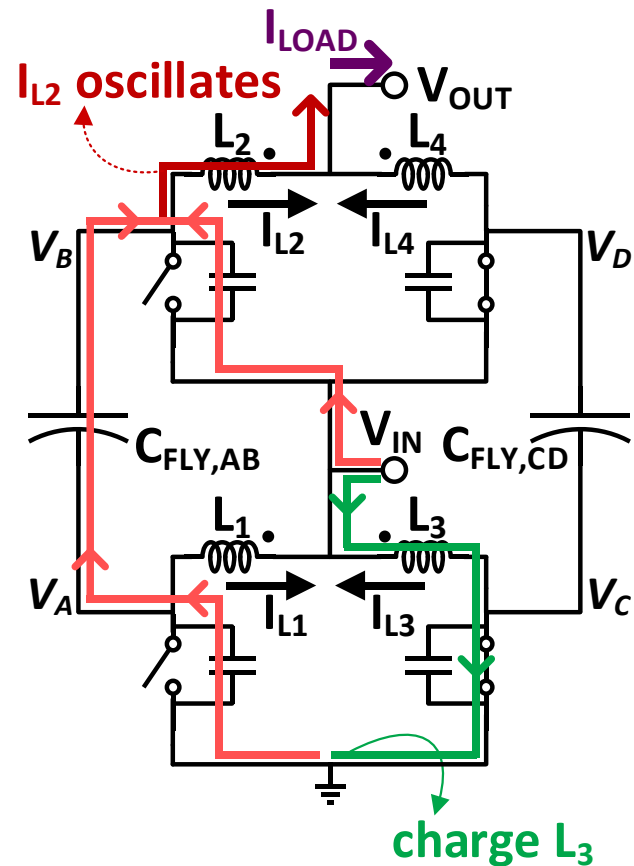

□ Φ_{1B} : L_3 charging, L_2 delivering I_{LOAD}



Operating Principles

Phase Φ_{2A}

 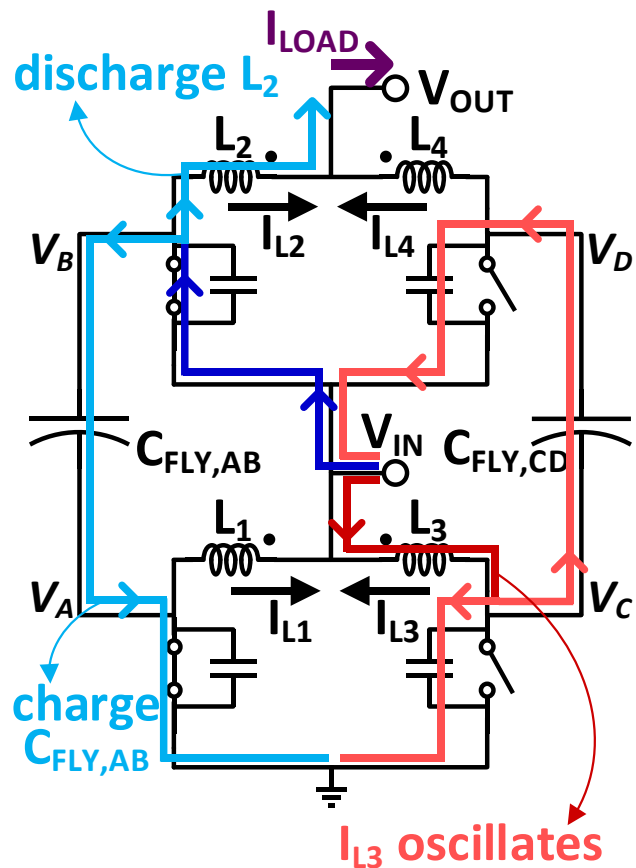

□ Φ_{2A} : L₃ energizing both oscillators, L₂ delivering I_{LOAD}


Operating Principles

  


□ Φ_{2B} : L_1 charging, L_4 delivering I_{LOAD}

On-chip Transformer Design

co-planar ground shield




 


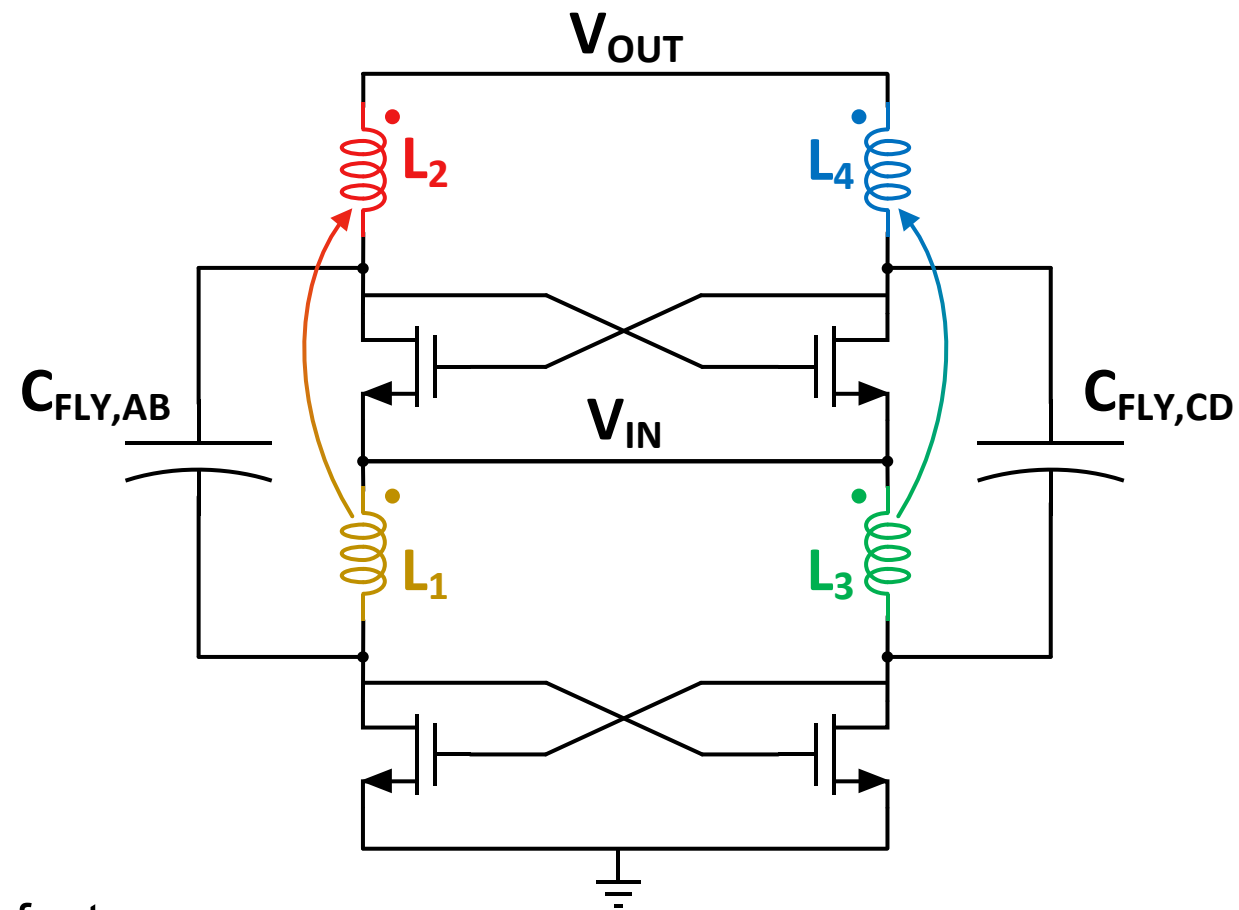- Interleaved loop structure
- Maximize $K_v = K_{12} = K_{34}$
- Minimize $K_h = K_{13} = K_{24}$
- Co-planar ground shield to improve the quality factor




On-chip Transformer Design

co-planar ground shield

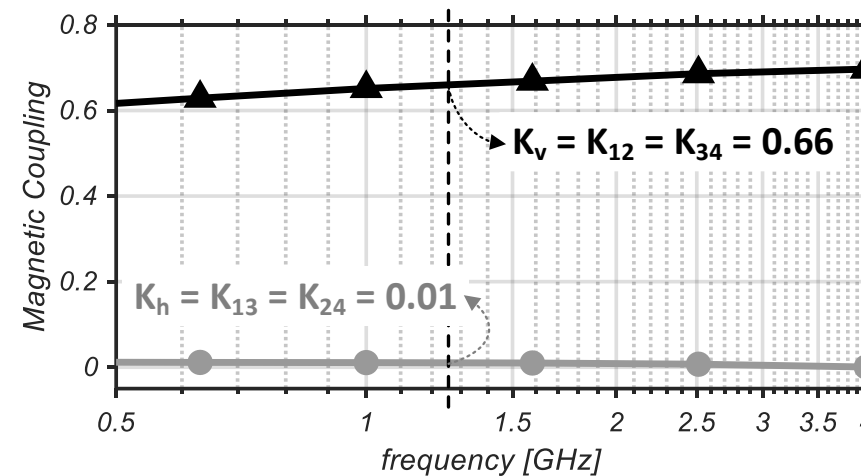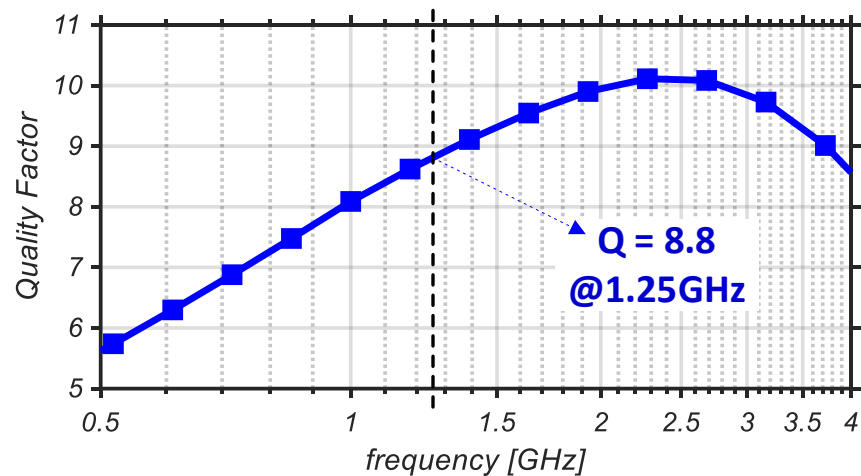
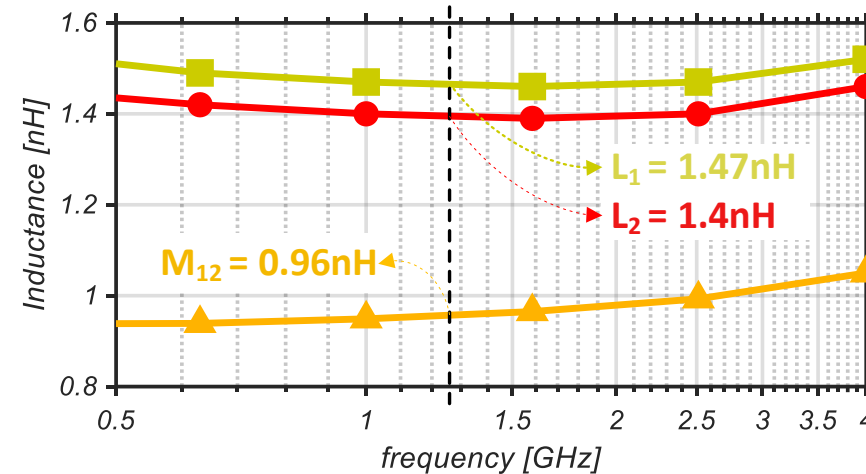
 


Duty cycling scheme for light load

 


- Footer NMOS placed to switch ON and OFF the oscillators

Duty cycling scheme for light load

   


- During the ON state power is delivered to VOUT



Duty cycling scheme for light load

 

EN = 1
Oscillators ON

 


EN = 0
Oscillators OFF

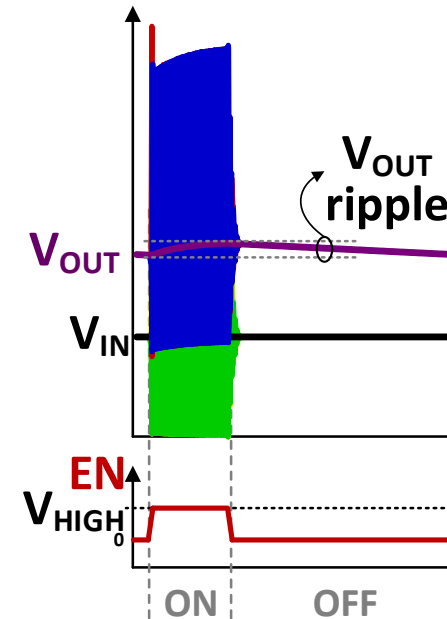 


- During the OFF state no power is delivered to the output



Duty cycling scheme for light load

 

EN = 1
 Oscillators ON




 


EN = 0
 Oscillators OFF

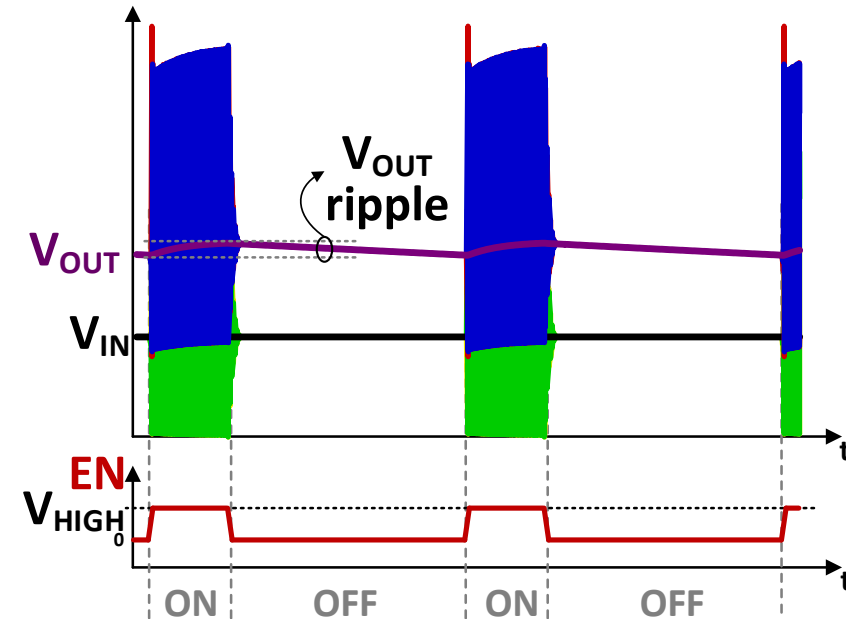 





- The duty cycling reduces power losses in light load conditions

Duty cycling scheme for light load

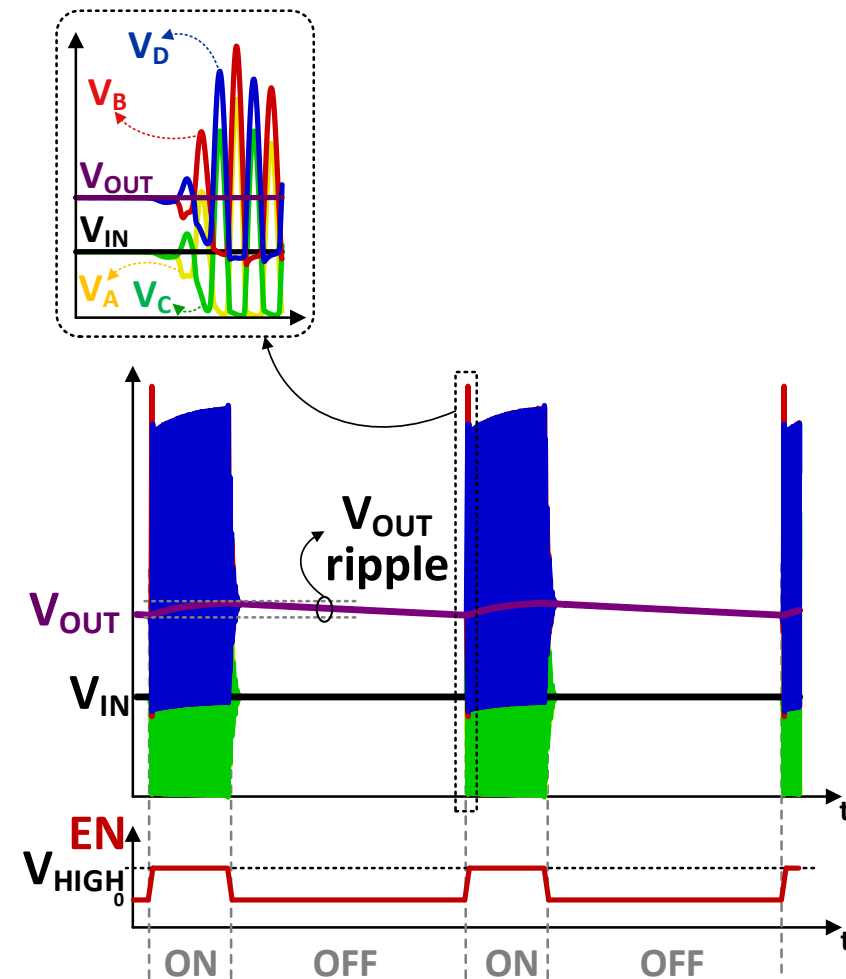  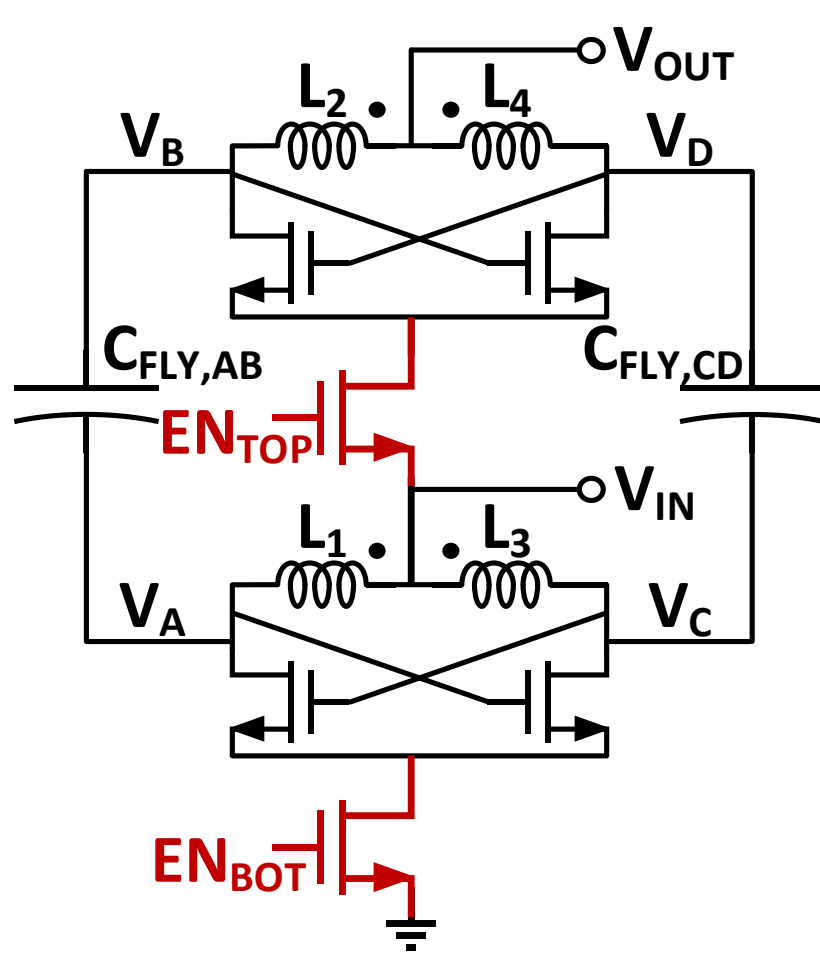





- Oscillators are switched ON and they start to resonate

Duty cycling scheme for light load

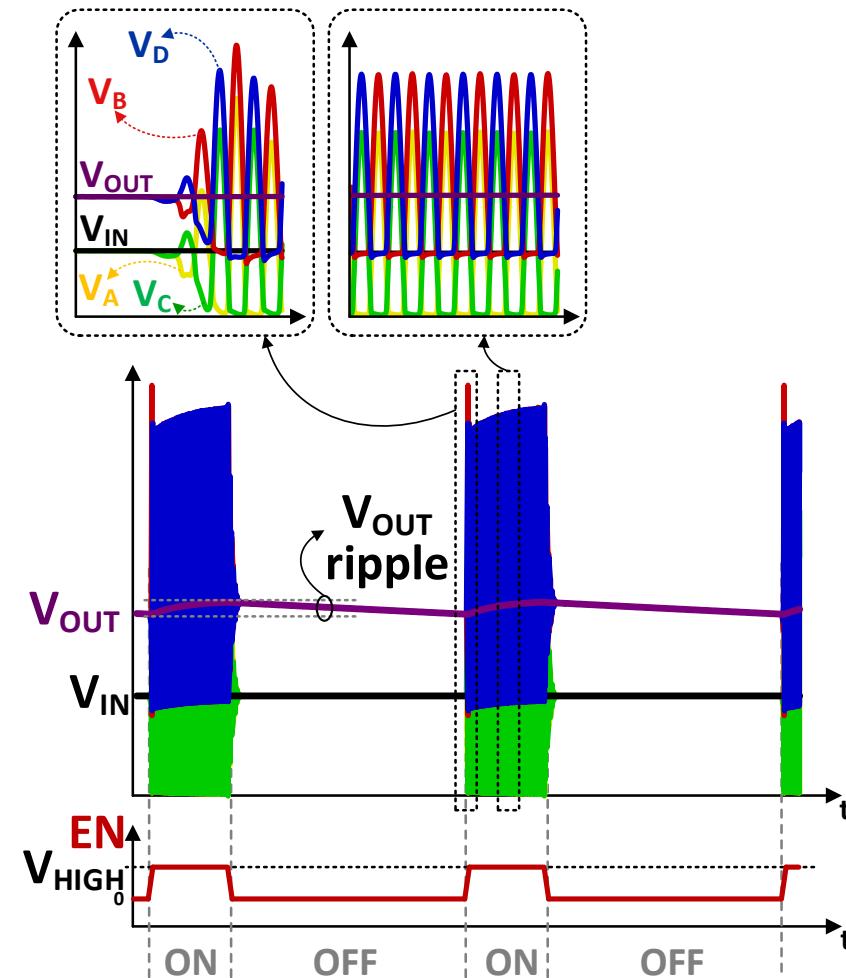   



□ Oscillators fully ON

Duty cycling scheme for light load

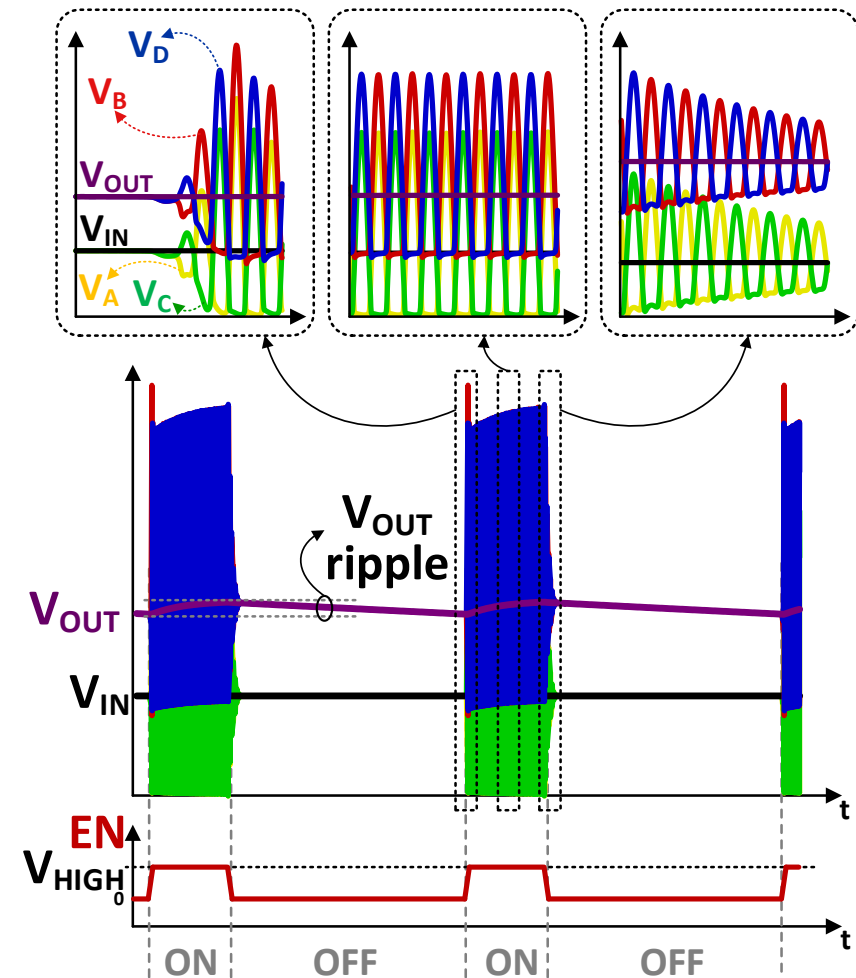   

□ Oscillation dying out

Chip Micrograph

  

□ High Efficiency

- $L_{\text{TOT}} = 7.8\text{nH}$ coupled
- $C_{\text{FLY,TOT}} = 458\text{pF}$


□ High Power Density

- $L_{\text{TOT}} = 3.1\text{nH}$ coupled
- $C_{\text{FLY,TOT}} = 152\text{pF}$


180nm bulk CMOS process

Measurement Result


Full Load

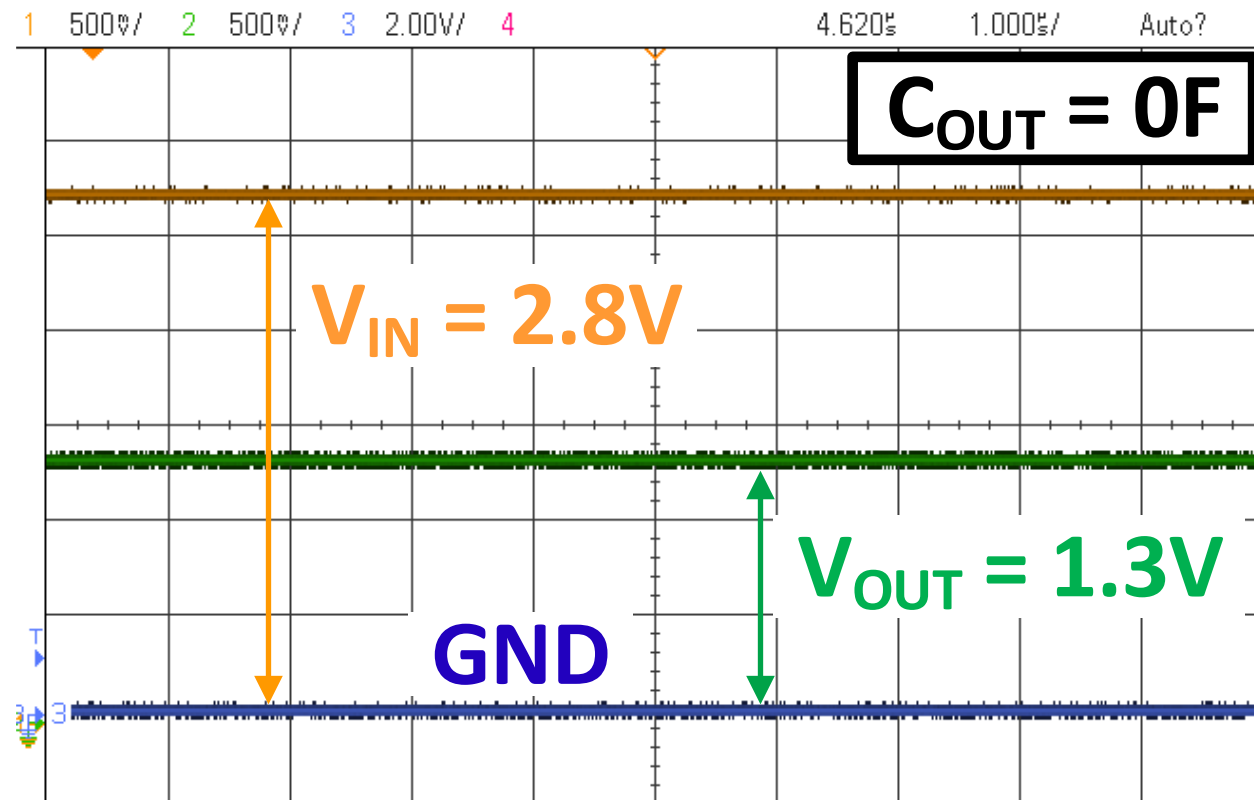


Duty Cycled

 

Measurement Results - Full Load

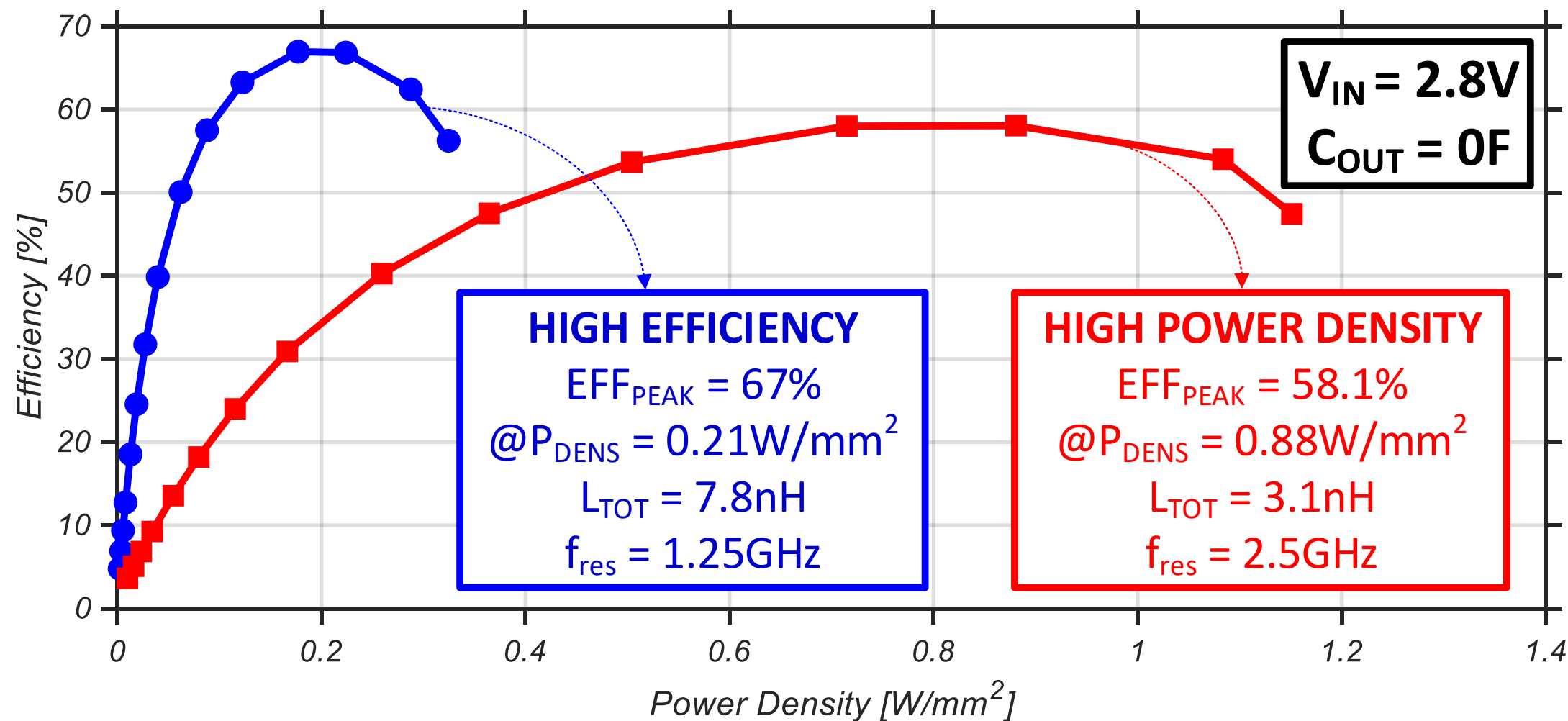

Measurement Results - Duty Cycled

 

Comparison Table

	Godycki ESSCIRC '14	Tang ISSCC '19	Schaef ISSCC '19	Renz ISSCC '19	McLaughlin ISSCC '20	This Work HIGH EFF	This Work HIGH PD
Topology	3-level Buck	SIC	Buck	ReSC	ReSC	EM-coupled class-D LC	EM-coupled class-D LC
Technology	65nm	65nm	14nm	130nm	180nm	180nm	180nm
f_{SW} (GHz)	not reported	0.45	0.07	0.0355	0.0475	1.25	2.5
V_{IN} (V)	1.8	1.2	1.6	3.0 - 4.5	2.4 - 4.4	1.0 – 3.6	1.0 – 3.0
V_{OUT} (V)	0.7	0.6 - 0.9	1.2	1.5 - 1.8	1.0-2.2	0.4 – 1.6	0.4 – 1.3
L_{TOT} (nH)	2 x 1.5	0.85	2.5 package	9	7.7 coupled	7.8 coupled	3.1 coupled
$C_{FLY,TOT}$ (nF)	2 x 1.5	1.72	-	2x1.0	2x 1.7	2x 0.229	2x 0.076
C_{IN} (nF)	not reported	not reported	not reported	0.18+off-chip	7	0	0
C_{OUT} (nF)	1.9	3.1	10 + off-chip	10	7	0	0
Area (mm ²)	2.09	0.65	2.16	7.83	8.93	1.61	0.37
Peak Eff (%) @ P_{DENS} (W/mm ²)	64 0.067	78 0.55	88 0.28	85.5 0.033	85.5 0.053	67 0.21	58.1 0.88
Peak P_{DENS} (W/mm ²) @Eff (%)	0.067 64	0.73 74.6	0.28 88	0.033 85	0.097 74.5	0.30 65.2	1 57.5

Comparison Table

	Godycki ESSCIRC '14	Tang ISSCC '19	Schaef ISSCC '19	Renz ISSCC '19	McLaughlin ISSCC '20	This Work HIGH EFF	This Work HIGH PD
Topology	3-level Buck	SIC	Buck	ReSC	ReSC	EM-coupled class-D LC	EM-coupled class-D LC
Technology	65nm	65nm	14nm	130nm	180nm	180nm	180nm
f_{SW} (GHz)	not reported	0.45	0.07	0.0355	0.0475	1.25	2.5
V_{IN} (V)	1.8	1.2	1.6	3.0 - 4.5	2.4 - 4.4	1.0 – 3.6	1.0 – 3.0
V_{OUT} (V)	0.7	0.6 - 0.9	1.2	1.5 - 1.8	1.0-2.2	0.4 – 1.6	0.4 – 1.3
L_{TOT} (nH)	2 x 1.5	0.85	2.5 package	9	7.7 coupled	7.8 coupled	3.1 coupled
$C_{FLY,TOT}$ (nF)	2 x 1.5	1.72	-	2x1.0	2x 1.7	2x 0.229	2x 0.076
C_{IN} (nF)	not reported	not reported	not reported	0.18+off-chip	7	0	0
C_{OUT} (nF)	1.9	3.1	10 + off-chip	10	7	0	0
Area (mm ²)	2.09	0.65	2.16	7.83	8.93	1.61	0.37
Peak Eff (%) @ P_{DENS} (W/mm ²)	64 0.067	78 0.55	88 0.28	85.5 0.033	85.5 0.053	67 0.21	58.1 0.88
Peak P_{DENS} (W/mm ²) @Eff (%)	0.067 64	0.73 74.6	0.28 88	0.033 85	0.097 74.5	0.30 65.2	1 57.5

Comparison Table

	Godycki ESSCIRC '14	Tang ISSCC '19	Schaef ISSCC '19	Renz ISSCC '19	McLaughlin ISSCC '20	This Work HIGH EFF	This Work HIGH PD
Topology	3-level Buck	SIC	Buck	ReSC	ReSC	EM-coupled class-D LC	EM-coupled class-D LC
Technology	65nm	65nm	14nm	130nm	180nm	180nm	180nm
f_{SW} (GHz)	not reported	0.45	0.07	0.0355	0.0475	1.25	2.5
V_{IN} (V)	1.8	1.2	1.6	3.0 - 4.5	2.4 - 4.4	1.0 – 3.6	1.0 – 3.0
V_{OUT} (V)	0.7	0.6 - 0.9	1.2	1.5 - 1.8	1.0-2.2	0.4 – 1.6	0.4 – 1.3
L_{TOT} (nH)	2 x 1.5	0.85	2.5 package	9	7.7 coupled	7.8 coupled	3.1 coupled
$C_{FLY,TOT}$ (nF)	2 x 1.5	1.72	-	2x1.0	2x 1.7	2x 0.229	2x 0.076
C_{IN} (nF)	not reported	not reported	not reported	0.18+off-chip	7	0	0
C_{OUT} (nF)	1.9	3.1	10 + off-chip	10	7	0	0
Area (mm ²)	2.09	0.65	2.16	7.83	8.93	1.61	0.37
Peak Eff (%) @ P_{DENS} (W/mm ²)	64 0.067	78 0.55	88 0.28	85.5 0.033	85.5 0.053	67 0.21	58.1 0.88
Peak P_{DENS} (W/mm ²) @Eff (%)	0.067 64	0.73 74.6	0.28 88	0.033 85	0.097 74.5	0.30 65.2	1 57.5

Conclusion

□ Proposed converter architecture

- Fully Integrated DC-DC converter
- Adiabatic switching of C_{BOT} & C_G enabling GHz-range f_{SW}
- No timing, shifters and bootstrap circuitry needed
- No load capacitor needed in full load operation

□ Performance

- 1 W/mm² peak power density
- Wide 70μW – 0.5W load range with duty-cycled operation

Key References

- C. Rindfleisch et al., "A One-Step 325V to 3.3-to-10V 0.5W Resonant DC-DC Converter with Fully Integrated Power Stage and 80.7% Efficiency," *ISSCC*, pp. 194- 195, Feb. 2020.
- N. Butzen et al., "A 94.6%-efficiency fully integrated switched-capacitor DC-DC converter in baseline 40nm CMOS using scalable parasitic charge redistribution," *ISSCC*, pp. 220-221, Feb. 2016.
- C. Schaef et al., "A Variable-Conversion-Ratio 3-Phase Resonant Switched Capacitor Converter with 85% Efficiency at 0.91W/mm² Using 1.1nH PCB-Trace Inductors," *ISSCC*, pp. 360- 361, Feb. 2015.
- P. H. McLaughlin et al., "A Fully Integrated Resonant Switched-Capacitor Converter with 85.5% Efficiency at 0.47W Using On-Chip Dual-Phase Merged-LC Resonator," *ISSCC*, pp. 192-193, Feb. 2020.
- W. Godycki, B. Sun, and A. Apsel, "Part-Time Resonant Switching for Light Load Efficiency Improvement of a 3-Level Fully Integrated Buck Converter," *ESSCIRC*, pp. 163-166, Sept. 2014.
- N. Tang et al., "8.4 Fully Integrated Buck Converter with 78% Efficiency at 365mW Output Power Enabled by Switched-Inductor Capacitor Topology and Inductor Current Reduction Technique," *ISSCC*, pp. 152-153, Feb. 2019.
- P. Renz et al., "8.6 A Fully Integrated 85%-Peak-Efficiency Hybrid Multi Ratio Resonant DC-DC Converter with 3.0-to-4.5V Input and 500μA -to-120mA Load Range," *ISSCC*, pp. 156-157, Feb. 2019.
- C. Schaef et al., "8.5 A Fully Integrated Voltage Regulator in 14nm CMOS with Package-Embedded Air-Core Inductor Featuring Self-Trimmed, Digitally Controlled Variable On-Time Discontinuous Conduction Mode Operation," *ISSCC*, pp. 154-155, Feb. 2019.