

High Efficiency Reconfigurable Monolithic Switched-Capacitor DC-DC Converter

Man-Kay Law (羅文基)

Institute of Microelectronics
State Key Laboratory of
Analog and Mixed-Signal VLSI
(University of Macau)

微電子研究院

模擬與混合信號超大規模集成電路

國家重點實驗室 (澳門大學)



澳門大學
UNIVERSIDADE DE MACAU
UNIVERSITY OF MACAU





Outline

- Background and Motivation
- Algebraic Series-Parallel (ASP)-based Boost Topology
- Algorithmic Voltage-Feed-In (AVFI) Buck/Boost Topology
- Summary

Powering the IoE Devices


■ Plentiful Devices Required for IoE Applications

  - Sense
- Measure
- Identify
- Monitor
- Connect
- Control
- Analyze
- Execute




Billions of “things” connected together

 Power Management with Energy Harvesting Sources




 - **Wide Input Range**
- **Switched-Capacitor (SC) for Power Conversion**
 - ✓ **Full integration**
 - ✓ **Fine-grained VCR (FVCR)**
 - ✓ **High efficiency**
 - ✓ **High power density**




Conduction/Parasitic Loss in SC Power Stage

 - **Conduction loss:** Slow switching (R_{SSL})
Charge sharing loss: Energy loss occurs when there is charge transferred between two capacitors.




 - **Conduction loss:** Fast switching (R_{FSL})
Switch on-impedance loss: Finite settling effect during Q_{tran} sharing.




Conduction/Parasitic Loss in SC Power Stage

➤ Total conduction loss

 




➤ Parasitic loss

 Due to charging and discharging the bottom-plate parasitic capacitance βC_i , where β depends on the choice of capacitor.




$$E_{ls,par} = \beta C_i \cdot \Delta V_{CB}^2$$


Fully Integrated FVCR SC Converter Comparison

   Topology	Series-Parallel	Dickson	Binary
	 $VCR = \frac{m}{m+n}, \{m, n \in \mathbb{Z}^+\}$	 $VCR = \left\{ \frac{1}{2}, \frac{1}{3}, \dots, \frac{1}{n+1} \right\}$	 $VCR = \frac{X}{2^n}, \{X = 1, 3, \dots, 2^n - 1\}$
VCR Flexibility	High	Low	Medium
Conduction Loss	VCR dependent	Optimal	Optimal
Parasitic Loss	Large	Optimal	Large

 
Fully Integrated FVCR SC Converter in bulk CMOS



 
Fully Integrated FVCR SC Converter in bulk CMOS



 Fully Integrated FVCR SC Converter in bulk CMOS



 Fully Integrated FVCR SC Converter in bulk CMOS




Outline


- Background and Motivation
- Algebraic Series-Parallel (ASP)-based Boost Topology
- Algorithmic Voltage-Feed-In (AVFI) Buck/Boost Topology
- Summary

Conventional FVCR SC SP Boost Converter


Integer VCR=2
(Dickson)

 

Fractional VCR=0.5
(series-parallel)

 

Cascaded VCR=2.5

 


➤ Cascaded Integer + Fractional Topology

- ✓ Intuitive implementation
- ✓ High flexibility with separate SC stages (e.g. Dickson + Series Parallel)
- ✓ Wide VCR generation for V_{IN} adaptation
- ✗ VCR Flexibility vs. conduction loss (R_{SSL})
- ✗ High parasitic loss

Conventional SP Topology



$$VCR = \frac{V_{OUT}}{V_{IN}} = K + \frac{m}{n}$$

$$K = 1, m = 1$$

 

- Parallel discharge (n branches) + Series charge (1 branch) with n capacitors
- Limited VCR generation: $VCR = \{\frac{1}{2}, \frac{1}{3}, \frac{1}{4}, \dots\}$
- High bottom-plate parasitic loss: $E_{par} \propto \sum (\Delta V_{CB, i})^2 = \sum \left(\frac{i \cdot V_{IN}}{n} \right)^2$

Conventional 2DSP Topology

  

- Fine-grained VCR using an $m \times n$ capacitor matrix
- High VCR flexibility as the capacitor matrix increases

Limitations of 2DSP

- Under the area-constrained condition:

Optimal R_{SSL} Expression

$$VCR = \frac{V_{OUT}}{V_{IN}} = K + \frac{m}{n}$$

$$a_{c,i} = \frac{Q_{c,i}}{Q_{out}}$$



$$*R_{SSL,opt} = \frac{(\sum |a_{c,i}|)^2}{C_{TOT} f_s} = \frac{1}{C_{TOT} f_s} \left(\frac{Kn + m - 1}{n} \right)^2$$

2DSP R_{SSL} Expression

$$R_{SSL,2DSP} = \frac{1}{C_{TOT} f_s} (m + K - 1)^2$$

→ $R_{SSL,2DSP} > R_{SSL,opt}$ except for $m=1$

  - Also, large parasitic loss still unresolved




[M. D. Seeman, TPEL'08]

ASP VCR Elaboration

■ 2DSP-Based Topology ($m \times n$)

 
$$V_{OUT} = V_{IN} + \underbrace{\left(m \times \frac{V_{IN}}{n} \right)}_{\text{Fractional}} + \underbrace{(K - 1)V_{IN}}_{\text{Integer}}$$



ASP VCR Elaboration

■ 2DSP-Based Topology ($m \times n$)
 
$$V_{OUT} = V_{IN} + \underbrace{\left(m \times \frac{V_{IN}}{n}\right)}_{\text{Fractional}} + \underbrace{(K-1)V_{IN}}_{\text{Integer}}$$



■ Proposed ASP VCR Elaboration ($2n-2$)


$$VCR = \frac{V_{OUT}}{V_{IN}} = K + \frac{m}{n}$$

$$nV_{OUT} = (Kn + m)V_{IN}$$

ASP VCR Elaboration

■ 2DSP-Based Topology ($m \times n$)
 
$$V_{OUT} = V_{IN} + \underbrace{\left(m \times \frac{V_{IN}}{n}\right)}_{\text{Fractional}} + \underbrace{(K-1)V_{IN}}_{\text{Integer}}$$



■ Proposed ASP VCR Elaboration ($2n-2$)

$$VCR = \frac{V_{OUT}}{V_{IN}} = K + \frac{m}{n}$$


$$nV_{OUT} = (Kn + m)V_{IN}$$

$$V_{OUT} = (Kn + m)V_{IN} - (n-1)V_{OUT}$$

ASP VCR Elaboration

■ 2DSP-Based Topology ($m \times n$)
 
$$V_{OUT} = V_{IN} + \underbrace{\left(m \times \frac{V_{IN}}{n}\right)}_{\text{Fractional}} + \underbrace{(K-1)V_{IN}}_{\text{Integer}}$$



■ Proposed ASP VCR Elaboration ($2n-2$)

$$VCR = \frac{V_{OUT}}{V_{IN}} = K + \frac{m}{n}$$

$$nV_{OUT} = (Kn + m)V_{IN}$$

$$V_{OUT} = (Kn + m)V_{IN} - (n-1)V_{OUT}$$

$$V_{OUT} = KV_{IN} + (n-m-1)(K-1)V_{IN} + mKV_{IN} + (n-1)(V_{IN} - V_{OUT})$$


Number of unit capacitors · Sustained voltage

ASP Operation

■ Proposed Implementation for the VCR Expression


$$V_{OUT} = \underbrace{KV_{IN}}_{\text{Phase 2}} + \underbrace{(n - m - 1)(K - 1)V_{IN}}_{\text{Phase 1}} + \underbrace{mKV_{IN}}_{\text{Phase 1}} + \underbrace{(n - 1)(V_{IN} - V_{OUT})}_{\text{Phase 1}}$$

Algebraic series-parallel stage

 

Integer Level Generation in ASP



Algebraic series-parallel stage

 

Dickson stage examples:

Generate $(K-1)V_{IN}$ for C_{x1} in ϕ_1

  
Generate $(K-1)V_{IN}$ for $C_{x(n-m-1)}$ in ϕ_1



For all C_x : total number of C_{Dx} , $N_{C_Dks,x} = (n - m - 1)(K - 2)$


Integer Level Generation in ASP

Algebraic series-parallel stage

 


Dickson stage examples:


Generate $(K-1)V_{IN}$ for C_{x1} in Φ_1

 

 Generate $(K-1)V_{IN}$ for $C_{x(n-m-1)}$ in Φ_1



Generate KV_{IN} for C_{ym} in Φ_1

 


For all C_x : total number of C_{Dx} , $N_{C_Dks,x} = (n - m - 1)(K - 2)$

For all C_y : $N_{C_Dks,y} = m(K - 1)$


Integer Level Generation in ASP

Algebraic series-parallel stage

 


Dickson stage examples:


Generate $(K-1)V_{IN}$ for C_{x1} in Φ_1

 

 
Generate $(K-1)V_{IN}$ for $C_{x(n-m-1)}$ in Φ_1



Generate KV_{IN} for C_{ym} in Φ_1

 

Generate KV_{IN} for $C_{z(n-1)}$ in Φ_2

 


For all C_x : total number of C_{Dx} , $N_{C_Dks,x} = (n - m - 1)(K - 2)$

For all C_y : $N_{C_Dks,y} = m(K - 1)$

For $C_{z(n-1)}$: $N_{C_Dks,z} = (K - 1)$

Complete ASP Topology Implementation

Algebraic series-parallel stage

 

No. of **ASP** cells:

$$N_{C_ASP} = 2n - 2$$

No. of **integer** cells:


$$N_{C_int} = Kn - 2n + m + 1$$

Total no. of cells:

$$N_{C_total} = Kn + m - 1$$


Dickson stage examples:

Generate $(K-1)V_{IN}$ for C_{x1} in Φ_1

 


For all C_x : total number of C_{Dx} , $N_{C_Dks,x} = (n - m - 1)(K - 2)$

 Generate $(K-1)V_{IN}$ for $C_{x(n-m-1)}$ in Φ_1




Generate KV_{IN} for C_{ym} in Φ_1

 

For all C_y : $N_{C_Dks,y} = m(K - 1)$


Generate KV_{IN} for $C_{z(n-1)}$ in Φ_2

 

For $C_{z(n-1)}$: $N_{C_Dks,z} = (K - 1)$

Complete ASP Topology Implementation

Algebraic series-parallel stage

 

No. of **ASP** cells:

$$N_{C_ASP} = 2n - 2$$

No. of **integer** cells:


$$N_{C_int} = Kn - 2n + m + 1$$

Total no. of cells:


$$N_{C_total} = Kn + m - 1$$

Dickson stage examples:


Generate $(K-1)V_{IN}$ for C_{x1} in Φ_1

 

 
Generate $(K-1)V_{IN}$ for $C_{x(n-m-1)}$ in Φ_1



Generate KV_{IN} for C_{ym} in Φ_1

 

Generate KV_{IN} for $C_{z(n-1)}$ in Φ_2

 


$$R_{SSL,ASP} = R_{SSL,opt}$$

$$= \frac{1}{C_{TOT}f_s} \left(\frac{Kn + m - 1}{n} \right)^2$$

ASP topology attains optimal R_{SSL}

ASP Topology Design Framework

 


$p_i = \{0,1\}$ is a design parameter $N_F = 2n - 2$

Capacitor voltage balance:

$$\begin{aligned}
 & \underbrace{(K - p_1)V_{IN} + (V_{IN} - V_{OUT}) + (K - p_3)V_{IN} + (V_{IN} - V_{OUT})}_{\phi_1} \\
 & + \dots + \underbrace{(K - p_{N_F-1})V_{IN} + (V_{IN} - V_{OUT})}_{\phi_2} = \underbrace{V_{OUT} - KV_{IN}}_{\phi_2}
 \end{aligned}$$

ASP Topology Design Framework

 

$p_i = \{0,1\}$ is a design parameter $N_F = 2n - 2$

Capacitor voltage balance:

$$\begin{aligned} & \underbrace{(K - p_1)V_{IN} + (V_{IN} - V_{OUT}) + (K - p_3)V_{IN} + (V_{IN} - V_{OUT})}_{\Phi_1} \\ & + \dots + \underbrace{(K - p_{N_F-1})V_{IN} + (V_{IN} - V_{OUT})}_{\Phi_2} = \underbrace{V_{OUT} - KV_{IN}}_{\Phi_2} \end{aligned}$$

$$VCR_{ASP} = \frac{V_{OUT}}{V_{IN}} = K + \overbrace{\frac{N_F - 2 \sum_{k=1}^{N_F/2} p_{2k-1}}{N_F + 2}}^{m/n}$$

$$\because N_F = 2n - 2$$


$$\because \sum p_i = n - m - 1 \text{ with optimal } R_{SSL}$$

However, there can be different options for the result of $p_1, p_3, p_5 \dots$

➤ p_i selection for parasitic loss reduction

Determination of Parameter p_i

■ Strategy: Limit Bottom-plate Switching Voltage $|\Delta V_{CB}|$

 

$$(K-1)V_{IN} < V_{OUT} - V_{IN} < KV_{IN}$$

Constraint condition: $|\Delta V_{CBi}| < V_{IN}$



$$p_i (i \text{ is odd}) = \begin{cases} 1, & \left(\frac{i+1}{2}\right)\left(1 - \frac{m}{n}\right) > 1 + \sum_{k=0}^{(i-1)/2} p_{2k-1} \\ 0, & \left(\frac{i+1}{2}\right)\left(1 - \frac{m}{n}\right) < 1 + \sum_{k=0}^{(i-1)/2} p_{2k-1} \end{cases}$$


[Y. Jiang, JSSC'19]

$$|\Delta V_{CBi}| = \begin{cases} \left| \Delta V_{CB(i-1)} + \left(\frac{m}{n} + p_i\right) V_{IN} \right|, & (i \text{ is odd}) \\ \left| \Delta V_{CB(i-1)} - V_{IN} \right|, & (i \text{ is even}) \end{cases}$$

Loss Comparison


■ ASP-based vs. 2DSP-based Topology (on conduction and parasitic Losses)

R_{SSL} vs. VCR

 


✓ $R_{SSL,ASP} < R_{SSL,2DSP}$
(except for $m = 1$)

Parasitic Loss vs. VCR
(fixed V_{IN})

 


Parasitic Loss vs. VCR
(fixed V_{OUT})

 

✓ ASP-based ones achieve lower parasitic loss
in both fixed V_{IN} and V_{OUT} cases.

ASP-based Topology Example

 

Step 1

Targeted VCR:

$$5:7 \rightarrow K = 1, m = 2, n = 5$$

$$5:12 \rightarrow K = 2, m = 2, n = 5$$

Step 2

No. of ASP cells:

$$N_F = 2n - 2$$

$\rightarrow$ 8 cells for ASP

Step 3

Determine p_i


$p_i (i \text{ is odd})$

$$= \begin{cases} 1, & \left(\frac{i+1}{2}\right) \left(1 - \frac{m}{n}\right) > 1 + \sum_{k=0}^{(i-1)/2} p_{2k-1} \\ 0, & \left(\frac{i+1}{2}\right) \left(1 - \frac{m}{n}\right) < 1 + \sum_{k=0}^{(i-1)/2} p_{2k-1} \end{cases}$$

ASP-based Topology Example


ASP Framework for $m/n = 2/5$

 $\rightarrow p_{1,3,5,7} = \{0 \ 1 \ 0 \ 1\}$



ASP-Based 5:7 ($K = 1$)

By reordering the cell sequence

 

$$\frac{\Delta V_{CB}}{V_{IN}} = \left\{ \frac{2}{5}, -\frac{3}{5}, -\frac{1}{5}, \frac{1}{5}, -\frac{4}{5}, -\frac{2}{5} \right\}$$


Notice:

With $K = 1$, C_3 and C_7 in the framework are simply eliminated.


ASP-based Topology Example

ASP Framework for $m/n = 2/5$

 $\rightarrow p_{1,3,5,7} = \{0 \ 1 \ 0 \ 1\}$




ASP-Based 5:7 ($K = 1$)

 


ASP-Based 5:12 ($K = 2$)

 With $K > 1$, no cell should be eliminated.




ASP-based Boost Converter Design Overview

 - Fully integrated in 65-nm bulk CMOS using 1-V core devices
- 7 reconfigurable rational boost VCRs (from 1:1.25 to 1:5)
- V_{IN} : 0.25~1V, $V_{OUT} = 1V$
- Dual-branch interleaving architecture
- Adaptive bootstrapping (ABS) switch driving circuits



Active area: 0.54mm²

 Total $C_{fly} \sim 3nF$ using MIM+MOS capacitors




Power Stage Reconfiguration Modes Summary

■ 7 Boost Topologies






Fractional Part
(ASP)

Integer Part
(Dickson)

 

Power Cell Implementation (C_1)

C₁ cell (0° branch)

     


$D_{VIN<2:0>} = 000 \sim 110 \rightarrow VCR = 4:5 \sim 1:5$

- ***Signals from state logics and D_{VIN}***
- ***LV power switches***
- ***Supports dual-branch operations***

Working Principle of Adaptive Bootstrapping Driver


Active State (en=1, $\overline{en}=0$)

 

$$V_{D,0} = V_{S,0} = V_{pass}$$


$$V_{D,180} \neq V_{S,180}$$
 
$$\text{Min}(V_{D,180}, V_{S,180}) = V_{b_L}$$




Working Principle of Adaptive Bootstrapping Driver

Disable State ($en=0, \overline{en}=1$)

 


$$V_{D,0} \neq V_{S,0}$$

$$V_{D,180} \neq V_{S,180}$$






 


 Measured Conversion Efficiency over V_{IN}



➤ **Peak efficiency of 80% at 2:3 is attained in heavy load cases with $V_{OUT} = 1V$**

      Converter Operating Frequency and Output Waveform



➤ V_{IN} vs. f_s at different R_L and VCR with $V_{OUT} = 1V$

➤ Measured V_{OUT} for 4:5 and 2:3 without using off-chip filtering capacitors.

Performance Summary and Comparison

	This work	JSSC'16 [15]	JSSC'15 [24]	JSSC'15 [30]	TVLSI'15 [13]	JSSC'17 [16]	JSSC'18 [34]	ISSCC'16 [35]
Technology	65nm CMOS	180nm CMOS	28nm FD-SOI	180nm CMOS	0.35 μ m CMOS	180nm CMOS	65nm CMOS	0.35 μ m HVCMOS
Conversion type	Boost	Boost	Boost	Boost	Boost	Boost	Buck-Boost	Buck-Boost
Topology type	ASP-based (ASP+Dickson)	SP-based (transposed SP)	Customized	Customized	SP-based (transposed SP)	Moving-sum (Dickson+SP)	AVFI	Binary Recursive
VCR type	Rational	Rational	Rational	Integer	Rational	Integer	Rational	Rational
Number of VCR	7	14	3	2	4	*22	13 (boost)	9 (boost)
VCR range	1.25 ~ 5	1.33 ~ 8	1.5 ~ 2.5	4 ~ 6	2 ~ 4 (boost)	10 ~ 31	1.1 ~ 7 (boost)	1.14 ~ 4 (boost)
Integrated C _{fly}	MOS + MIM	HD-MIM	MOS + MOM	MOS + MIM	Off-chip	N/R	MOS + MIM	MIM
V _{IN} Range [V]	0.25 ~ 1	0.45 ~ 3	1	1	1.4 ~ 3	0.25 ~ 0.65	0.26 ~ 1.3 (boost)	2 ~ 6 (boost)
V _{OUT} [V]	1	3.3	1.2 ~ 2.4	3 ~ 6	4.8	4	1.2	5
I _{OUT_MAX} [mA]	20.1	0.015	1	0.24	10	*0.001	21.7 (boost)	1.4 (boost)
η_{peak} [%]	#80	81	#88	58	82	60	83.2 (boost)	70.9 (boost)
P-density @ η_{peak} [mW/mm ²]	#22.7	*0.0174	#4.9	*2.4	N/A	*~0.0001	10.8 (boost)	*0.15 (boost)
Fully integrated	Yes	Yes	Yes	Yes	No	Yes	Yes	Yes

*Estimated from the corresponding literature


#Regulation control executed externally

Outline

- Background and Motivation
- Algebraic Series-Parallel (ASP)-based Boost Topology
- **Algorithmic Voltage-Feed-In (AVFI) Buck/Boost Topology**
- Summary

Cell Extraction from Existing Dickson Topologies


Existing Dickson Topologies (*Boost*)

 

- **Optimal** bottom plate switching (ΔV_{CB})
- **Limited** VCR of 1:N, (N-1):N

Basic Cell Extraction


Dickson Cell (DSC) (*Boost*)

 


- ΔV_{CB} : V_{IN} or $V_{OUT} - V_{IN}$
- **Inter-Cell Q-Transfer Path:**
Top Plate in Top Plate out (**TT**)
Bott. Plate in **Bott.** Plate out (**BB**)

Generating of Charge-path Folding Cell (QFC) (Boost)

Dickson Cell (DSC) (*Boost*)

 

Q-path Folding Cell (QFC) (*Boost*)

 


Cell Extension

■ Lacks VCR flexibility

- ΔV_{CB} : Internal-node dependent
- **Inter-Cell Q-Transfer Path: “Folded”**
Bottom Plate in Top Plate out (**BT**)
Top Plate in Bottom Plate out (**TB**)

 Cell-Based Topology Design Concept (*Boost*)



Cell Parameterization (*Boost*): b_i & m_i

V_{OUT} feed-in coefficient: $b_i \Rightarrow b_i = 0$

$b_i = 1$





Q-folding (QF) coefficient: m_i

$$S_{i,o} = S_{i,l} + V_{IN} - b_i V_{OUT}$$

$$b_i = 0: S_{i,o} = S_{i,l} + V_{IN}$$

$$b_i = 1: S_{i,o} = S_{i,l} + V_{IN} - V_{OUT}$$

Unique cell configuration by b_i & m_i

    


DSC: $m_i = 0$


QFC: $m_i = 1$

Cell Parameter Summary (*Buck/Boost*): a_i, b_i, m_i

Basic Power Cells:

 


Topology generation steps:

 


Cell Parameter Summary (*Buck/Boost*): a_i, b_i, m_i

Basic Power Cells:

 


Algorithmic Power Cell Model:

 


AV_{OUT}FI Topology Framework (*Boost*)
 
$$S_{i,0} = S_{i,1} + V_{IN} - b_i V_{OUT}$$



**Algorithmic
Power Cell Model**

 Algorithmic V_{OUT} feed-in (AV_{OUT}FI) Topology Framework



$$S_{i,0} = (1+i)V_{IN} - (\sum_{j=1}^i b_j)V_{OUT}$$

$$VCR = \frac{Y}{X} = \frac{V_{OUT}}{V_{IN}} = \frac{1+n}{1+\sum_{i=1}^{n-1} b_i}$$

AV_{OUT}FI Topology Framework (*Boost*)

Boost $X : Y$


$$*R_{SSL,min} = \frac{Y-1}{X}$$

$$\begin{aligned} R_{SSL,AVFI} &= \sum \left(\frac{Q_{Ci}}{Q_{OUT}} \right) \\ &= \frac{n}{1 + \sum_{i=1}^{n-1} b_i} \\ &= \frac{Y-1}{X} \\ &= R_{SSL,min} \end{aligned}$$

 *** Area-Constrained**

[M. D. Seeman, TPEL'08]

Algorithmic V_{OUT} feed-in (AV_{OUT}FI) Topology Framework




$$S_{i,0} = (1+i)V_{IN} - \left(\sum_{j=1}^i b_j \right) V_{OUT}$$

$$VCR = \frac{Y}{X} = \frac{V_{OUT}}{V_{IN}} = \frac{1+n}{1 + \sum_{i=1}^{n-1} b_i}$$

$AV_{OUT}FI$ Topology Framework (*Boost*)


Design Concept

With a VCR Target

 

Algorithm to
determine b_i & m_i

 
Algorithmic V_{OUT} feed-in ($AV_{OUT}FI$) Topology Framework



Generating a topology with reduced parasitic loss.

Algorithm for b_i Determination (*Boost*)

 Level Bounded Rule (LBR) (boost): $S_{1 \sim (n-1),0} \in (V_{SS}, V_{OUT})$.



Applying the **LBR**:

$$0 < S_{i,0} < V_{OUT}$$




b_i algorithm

$$b_i = \begin{cases} 1, & (1+b_1+\dots+b_{i-1})V_{CR} < i+1 \\ 0, & (1+b_1+\dots+b_{i-1})V_{CR} > i+1 \end{cases}$$

$$b_n = 0$$

Determination of m_i (*Boost*)

m_i b_i	0 (DSC)	1 (QFC)
0	$S_{i,I}$ $S_{i,O}$ V_{IN} V_{SS} (TT)	V_{IN} $S_{i,O}$ $S_{i,I}$ V_{SS} (BT)
1	V_{IN} V_{OUT} $S_{i,I}$ $S_{i,O}$ (BB)	$S_{i,I}$ V_{OUT} V_{IN} $S_{i,O}$ (TB)

 


C_1 implementation
solely depends on b_1 .
(identical for $m_1 = 0$ or 1)


$C_{2 \sim n}$ implementation depends on
both $b_{2 \sim n-1}$ & $m_{2 \sim n}$.
→ Explore m_i algorithm with
stage-by-stage ΔV_{CB} optimization.

Determination of m_i (*Boost*)

 - $S_{i,O} = S_{i,I} + V_{IN} - b_i V_{OUT} \rightarrow S_{i,O} > V_{IN}$ when $b_i = 0$



 
- $S_{i,O} = S_{i,I} + V_{IN} - b_i V_{OUT} \rightarrow S_{i,O} < V_{IN}$ when $b_i = 1$



Lower $\Delta V_{CB} \rightarrow m_i = b_{i-1} \oplus b_i \rightarrow C_{TOP} - C_{TOP}$ or $C_{BOT} - C_{BOT}$ Inter-cell Q-Transfer

Proposed AV_{OUT}FI Topology Summary (*Boost*)

*Topology
Model*

 

*Coefficients
Algorithm*

V_{OUT}FI Coefficient

$$b_i = \begin{cases} 1, & (1+b_1+\dots+b_{i-1})VCR < i+1 \\ 0, & (1+b_1+\dots+b_{i-1})VCR > i+1 \end{cases}$$

$$b_n = 0$$

QF Coefficient


$$m_i = b_{i-1} \oplus b_i, \quad m_1 = \text{either } 1 \text{ or } 0$$

Power Cell Table

$\begin{matrix} m_i \\ b_i \end{matrix}$	0 (DC)	1 (QFC)
0	V_{IN} V_{SS} (TT)	V_{IN} V_{SS} (BT)
1	V_{IN} V_{OUT} (BB)	V_{IN} V_{OUT} (TB)

Proposed AV_{IN}FI Topology Summary (*buck*)

Topology Model

 

Coefficients Algorithm

LBR (*buck*):

$$S_{1 \sim (n-1),0} \in (V_{SS}, V_{IN})$$

$$S_{i,0} = (1 + \sum a_{1 \sim i})V_{IN} - iV_{OUT}$$

$$0 < S_{i,0} < V_{IN}$$

V_{IN}FI Coefficient

$$a_i = \begin{cases} 1, & iVCR > 1 + a_1 + a_2 + \dots + a_{i-1} \\ 0, & iVCR < 1 + a_1 + a_2 + \dots + a_{i-1} \end{cases}$$

$$a_1 = 0$$

QF Coefficient


$$m_i = a_i \oplus a_{i+1}, \quad m_n = \text{either } 1 \text{ or } 0$$

Power Cell Table

m_i a_i	0 (DSC)	1 (QFC)
0	$S_{i,0}$ V_{SS} V_{OUT} (TT)	$S_{i,0}$ V_{SS} $S_{i,0}$ (TB)
1	V_{IN} V_{OUT} $S_{i,0}$ (BB)	V_{IN} $S_{i,0}$ $S_{i,0}$ (BT)

Proposed AVFI Topology Summary (*Buck/Boost*)

n-stage AVFI buck-boost topology

 

$$VCR = \frac{1 + \sum a_{1 \sim n}}{1 + \sum b_{1 \sim n}}$$

a_i, b_i, m_i for arbitrary VCR can be algorithmically determined

Buck:

$$a_1 = 0, b_{1 \sim n} = 1$$

$$a_i = \begin{cases} 1, & iVCR > 1 + a_1 + a_2 + \dots + a_{i-1} \\ 0, & iVCR < 1 + a_1 + a_2 + \dots + a_{i-1} \end{cases}$$

$$m_i = a_i \oplus a_{i+1}, m_n = X \text{ (1 or 0)}$$

Boost:

$$a_{1 \sim n} = 1, b_n = 0$$

$$b_i = \begin{cases} 1, & (1 + b_1 + \dots + b_{i-1})VCR < i + 1 \\ 0, & (1 + b_1 + \dots + b_{i-1})VCR > i + 1 \end{cases}$$

$$m_i = b_{i-1} \oplus b_i, m_1 = X \text{ (1 or 0)}$$

Proposed AVFI Example 7:4 (*Buck*)


1. Arbitrary **VCR** = 7:4
2. Number of cell **N_C**:
Buck: $N_C = p - 1$
Boost: $N_C = q - 1$
3. Calculate VFI coefficients a_i / b_i .
4. Calculate QF coefficient m_i .
5. Apply corresponding **power cell configurations** from the table with the calculated $a_i / b_i / m_i$.
6. Assign proper **switching phase** for all power stages.

1~2). VCR = 7:4 → number of cell **N_C** = 6.

3~4). Coefficients: buck → **b_{1~6}** = 1,

$$a_{1~6} = \{0 \ 1 \ 0 \ 1 \ 0 \ 1\} \rightarrow m_{1~6} = \{1 \ 1 \ 1 \ 1 \ 1 \ X\}$$

5~6). Topology implementation:

 



Q-Conduction Loss Comparison

$$M_{CON} = \left(\sum \frac{Q_{C,i}}{Q_{OUT}} \right)^2$$

◇ AVFI (24 VCRs)

[Jung ISSCC'16]
× NSC (3-stage)

  [Salem ISSCC'14]
[Lutz ISSCC'16]
□ RSC (4-stage)



Optimal conduction loss factor as in existing topologies.



Parasitic Loss Comparison

$$M_{PAR} = \frac{1}{M_{CON}} \sum \left[\left(\frac{Q_{C,i}}{Q_{OUT}} \right) \left| \frac{\Delta V_{CB}}{V_{IN}} \right|^2 \right]$$

◇ AVFI (24 VCRs)

[Jung ISSCC'16]
× NSC (3-stage)

  
[Salem ISSCC'14]
[Lutz ISSCC'16]
□ RSC (4-stage)



Improved parasitic loss factor than existing topologies.

Simulation Results & Comparison

 
Wide V_{IN} range buck-boost conversion by different topologies



$0.2\text{V} < V_{IN} < 2.3\text{V}$, $V_{OUT} = 1\text{V}$, $I_{load} = 20\text{mA}$
 $C_{Bot-par} = 8\%$, $A_{cap} = 1\text{mm}^2$




R_{SSL} : AVFI = NSC = RSC < S-P
 R_{PAR} : AVFI < NSC $\leq$ RSC < S-P

Converter Overview




 


- 10 main + 10 auxiliary cells
- VCRs: 11 buck + 13 boost
- Dual-branch interleaved
- 25MHz clock pulse-skipping modulation


Cells Partitioning Mode Summary

   

    - $C_{MC}:C_{AC} = 5:1$
- 7 partition modes with cascaded or parallel cells
- Support 24 VCRs
- Full cap. utilization
- # of cell reduction:
60 $\rightarrow$ 20




Chip Implementation

 


- 1~2) 10 MC C_{fly} (MIM + MOS) and C_{OUT} (MOS) for 0° and 180° branches
- 3~4) 10 AC C_{fly} (MIM + MOS) and C_{OUT} (MOS) for 0° and 180° branches
- 5~7) RSBDs + digital control
- 8~9) Power switches

 Measured Conversion Efficiency over V_{IN} ($V_{OUT} = 1V$)




Measured Efficiency over Output Power Range

Buck

 


Boost

 

- Max. $P_{OUT} > 80\text{mW}$ with buck 2:1

Measured Load Transient Waveforms

 $VCR = 6:5$, $f_s = 25\text{MHz}$, $V_{IN} = 1.32\text{V}$, $V_{OUT} > 1\text{V}$, $C_{L_EX} = 0\mu\text{F}$



Performance Summary and Comparison


	This work	D. Lutz ISSCC'16	C. K. Teh ISSCC'16	M. Saadat ASSCC'15	X. Hua CICC'15	J. Jiang JSSC'17
Technology	65nm CMOS	0.35 μ m HVCMOS	65nm CMOS	0.25 μ m CMOS	65nm CMOS	130nm CMOS
Conv. type	Buck-Boost	Buck-Boost	Buck-Boost	Buck-Boost	Buck-Boost	Buck
No. of VCR	11 buck + 13 boost	8 buck + 9 boost	5 buck + 1 boost	4 buck + 4 boost	3 buck + 3 boost	6 buck
Integrated C _{fly}	MOS + MIM	MIM	MOS + off-chip 1 μ F	MIM	N/R	Off-chip 4 μ F
V _{IN} [V]	0.22 ~ 2.4	2 ~ 13	0.85 ~ 3.6	0.6 ~ 2.4	0.5 ~ 3.3	1.6 ~ 3.3
V _{OUT} [V]	0.85 ~ 1.2	5	0.1 ~ 1.9	1.2 ~ 1.5	1	0.5 ~ 3
I _{OUT_MAX} [mA]	80.1	4	10	0.1	0.0033	120
η_{peak} [%]	Buck: 84.1 Boost: 83.2	Buck: 81.5 Boost: 70.9	Buck: 95.8 Boost: 90.5	76	70.4	91
P-den@ η_{peak} [mW/mm ²]	Buck: 13.2 Boost: 10.2	*Buck: 0.96 *Boost: 0.15	N/R	*0.062	*0.0069	N/A

* Estimated from the corresponding literature

Outline

- Background and Motivation
- Algebraic Series-Parallel (ASP)-based Boost Topology
- Algorithmic Voltage-Feed-In (AVFI) Buck/Boost Topology
- Summary

Summary

 

Acknowledgement

- Macau Science and Technology Fund (FDCT)
- Research Committee of University of Macau



科學技術發展基金
F | D | C | T



澳門大學
UNIVERSIDADE DE MACAU
UNIVERSITY OF MACAU

Thank you for your attention!

Man-Kay Law (MKLaw@um.edu.mo)