

Power Without Pain: High Power MMIC PA Design, the Pitfalls and how to Avoid Them

Michael Roberg


Qorvo, Inc.

QORVOTM

all around you



Background & Motivation

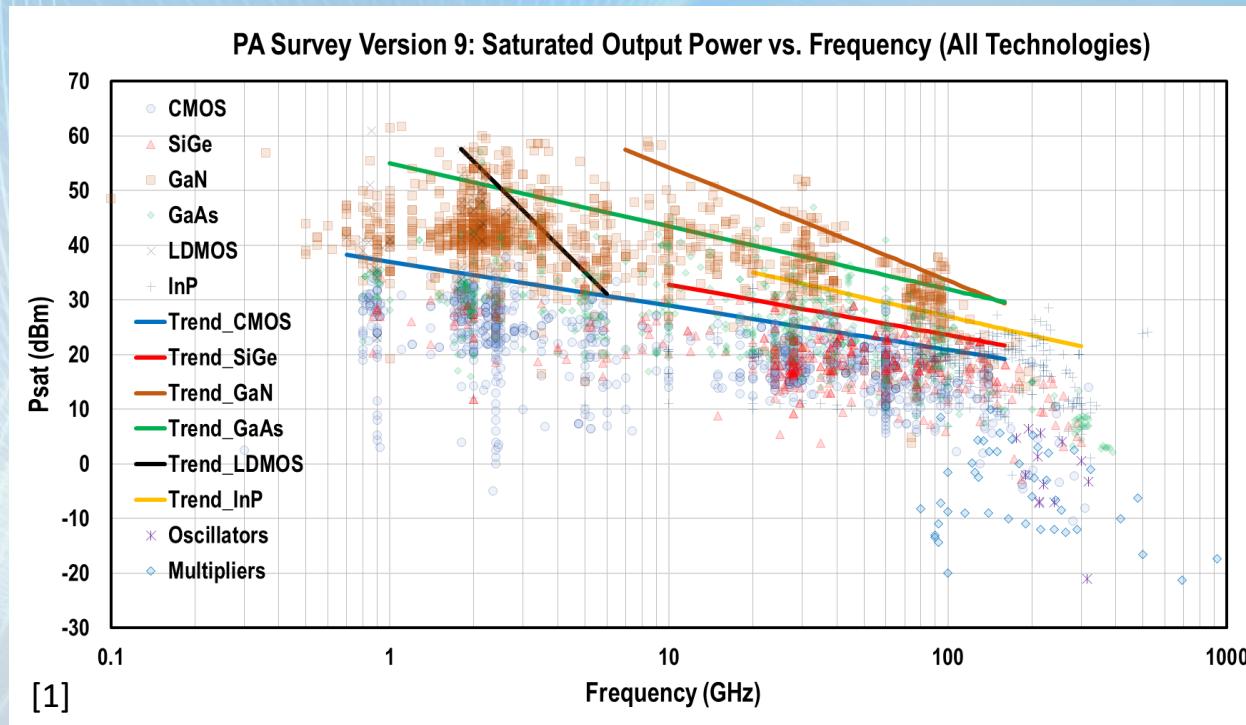

GaAs and GaN PAs Dominate Below 100 GHz

GaAs vs. GaN

- **Power:** GaN has higher maximum power density (>10x) mainly due to drain voltage, resulting in higher power MMICs
- **Efficiency:** Efficiency is similar between the technologies
- **Linearity:** GaAs is typically a more linear technology. GaN linearity is still a work in progress although some foundries are doing quite well
- **Frequency:** Relatively similar. Strong research thrust to push GaN to D-band
- **Thermal:** GaN can operate reliably at a higher channel temperature (typically 225°C) vs < 160°C typical in GaAs. GaN is typically grown on a SiC substrate, which has a higher thermal conductivity than GaAs
- **Matching:** GaAs is often easier to match (lower $R_p \times C_p$ product) due to lower drain voltage. Typical GaN has a knee voltage which is quite high precluding useful operation at a GaAs operating voltage (e.g. < 8V).
- **Cost:** GaN is more expensive than GaAs (~2X)
- **Schedule:** GaN typically takes longer than GaAs to process (~2X)

	GaAs	GaN
Power		✓
Efficiency	✓	✓
Linearity	✓	
Frequency	✓	✓
Thermal		✓
Matching	✓	
Cost	✓	
Schedule	✓	

GaN & GaAs MMIC PA Topologies

Most Common

Reactively Matched




Balanced

Non-Uniform
Distributed

Other

Least Common

Reactively Matched PA Topology

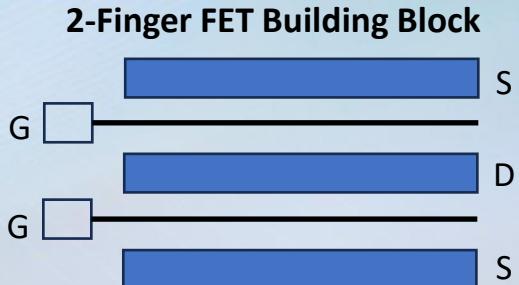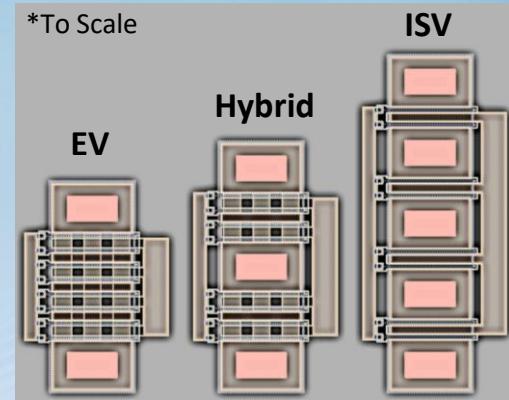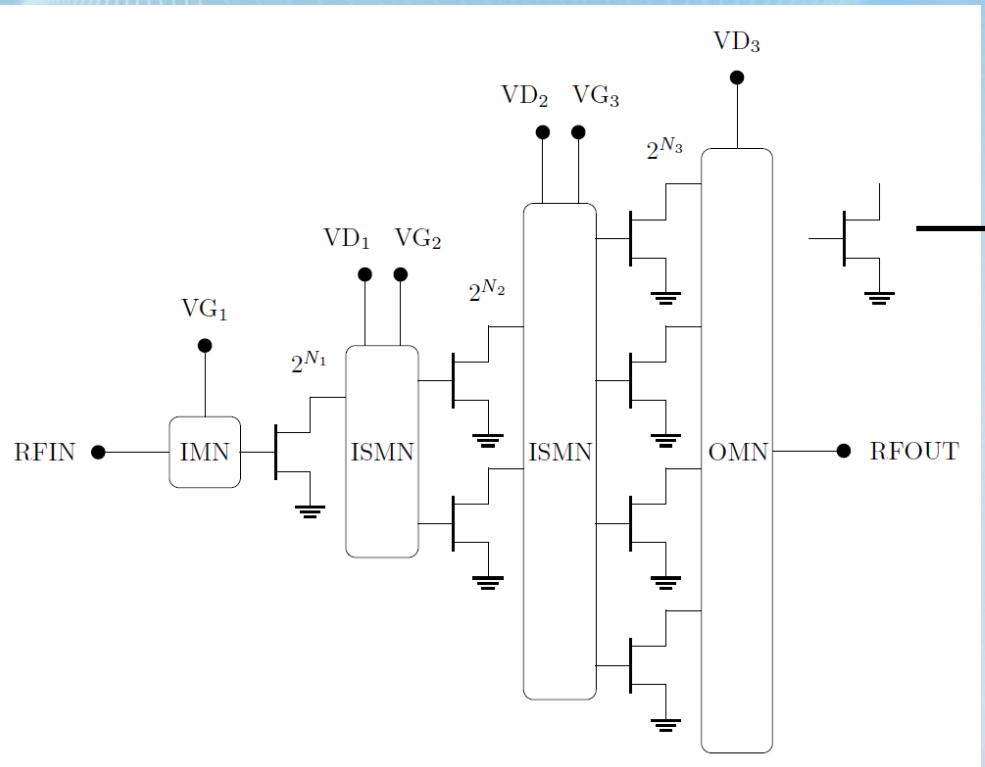


Why Reactive? Highest Power / PAE and Straightforward

Reactively Matched PA Design Procedure


Attack The Problem Backwards

- Design the Output Matching Network first
 - Typically the designer has an idea of the optimal load for desired performance parameters (e.g. power, PAE, etc)
 - Ensure the load to each device is uniform and the match is low loss to maximize power combining efficiency
- Once the OMN is designed, design the Inter-Stage Matching Network
 - Apply same techniques used to design the OMN
 - Ensure adequate drive margin
 - Often the most difficult network to design
- Keep working backwards to the Input Matching Network
 - Typically the easiest network to design
 - Optimize all networks to maximize performance

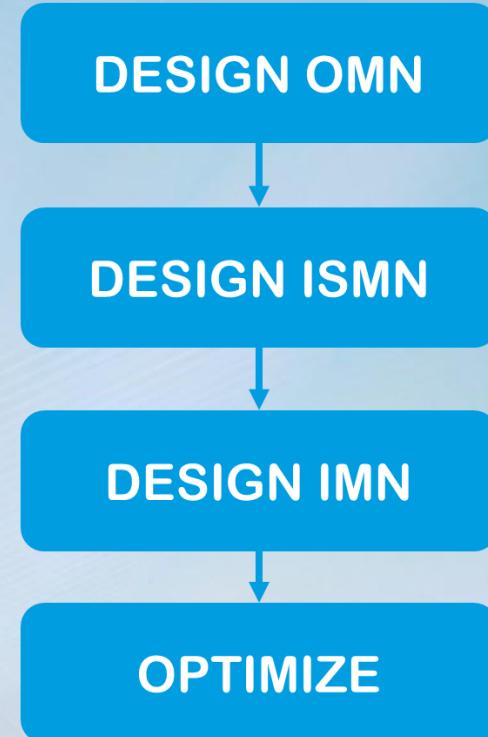


Reactively Matched MMIC PA Examples

[2] 400W S-Band

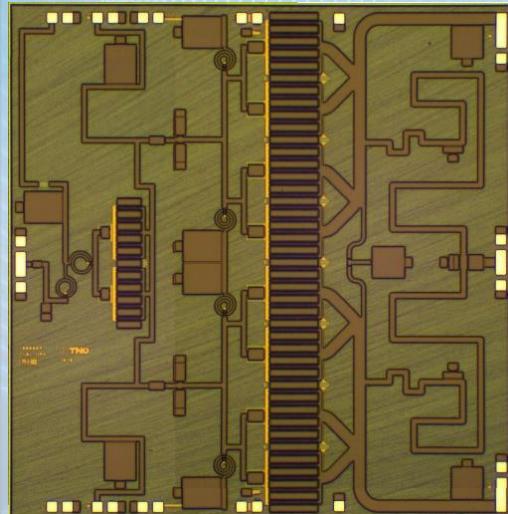


$V_D = 55V$, $L_G = 450nm$

[3] 100W X-Band

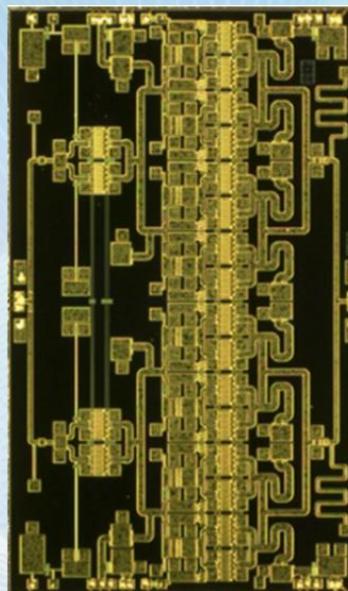


$V_D = 40V$, $L_G = 250nm$

[4] 50W Ku-Band

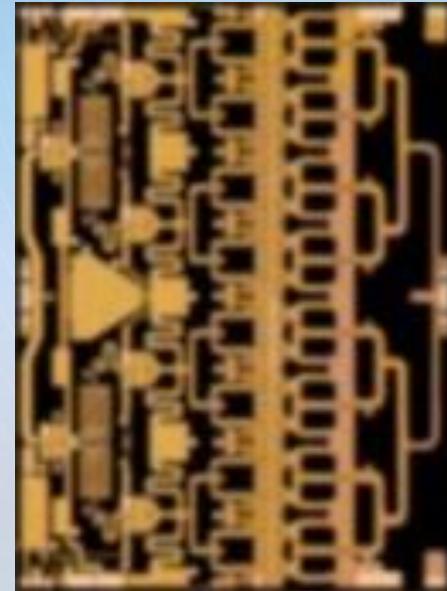

$V_D = 28V$, $L_G = 150nm$

[5] 40W Ka-Band


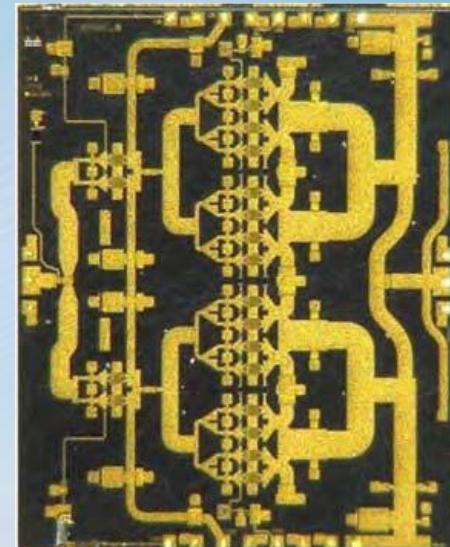


$V_D = 28V$, $L_G = 200nm$

*All die are not to scale

Balanced MMIC PA Topology

[6] Lange Coupler

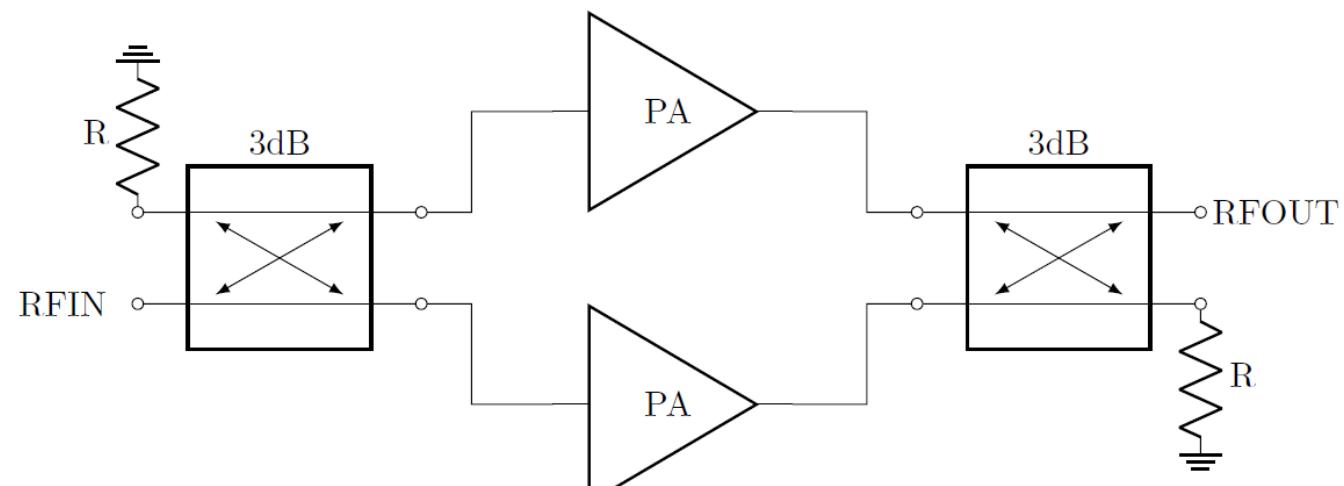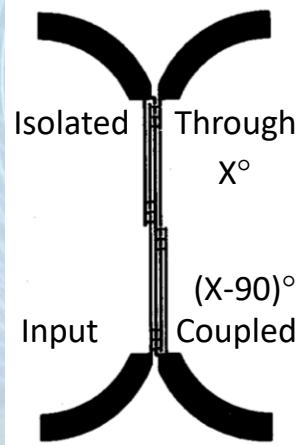

Why Balanced? Good Return Loss, Load Mismatch
Tolerance and 2-Way Combining

Balanced PA Design Procedure

1

Design 90°
Hybrid

2

Design
Core PA


3

Integrate


Hybrid is almost always a Lange Coupler

Balanced MMIC PA Examples


[7] 40W 4-18 GHz

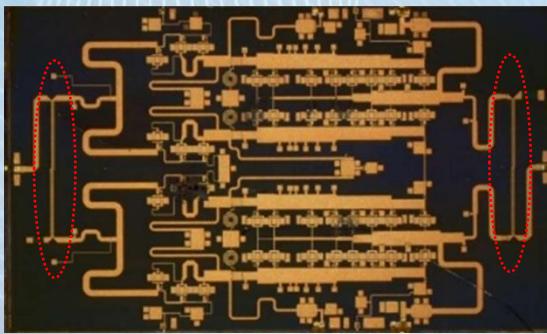


[8] 40W 27-31 GHz

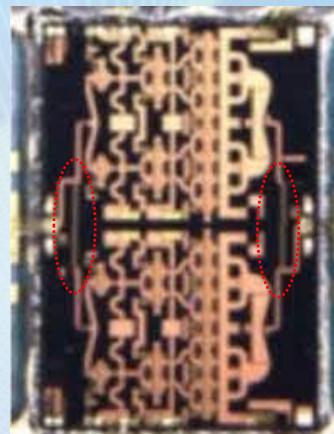

[7] 25W 32-38 GHz

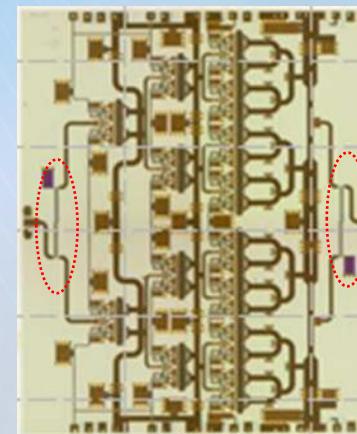


[9] 4W 74-80 GHz

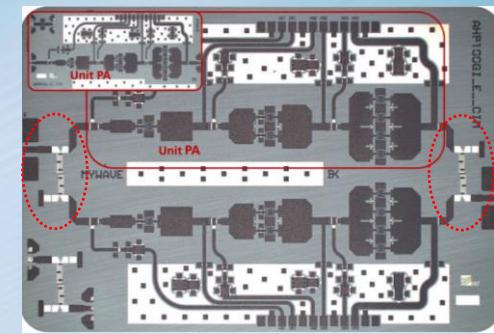

= Lange Coupler


Nonuniform Distributed MMIC PA Topology

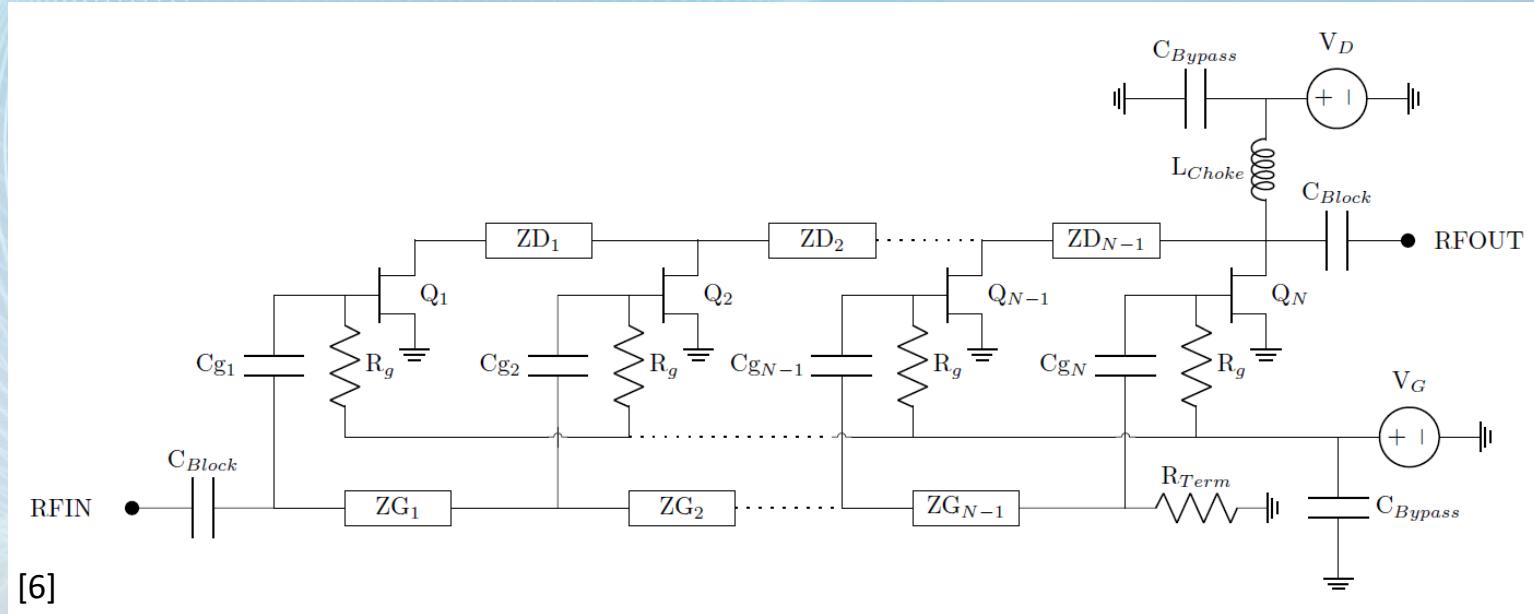


Why Distributed? Bandwidth and Load Tolerance

Nonuniform Distributed MMIC PA Examples


[10] 10W 1-8 GHz

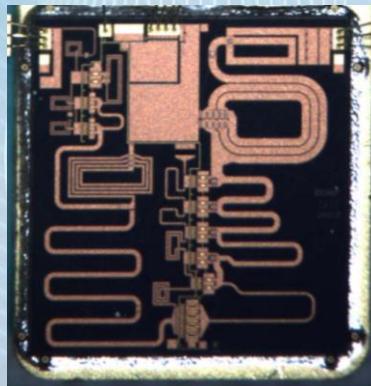


[11] 35W 4-18 GHz

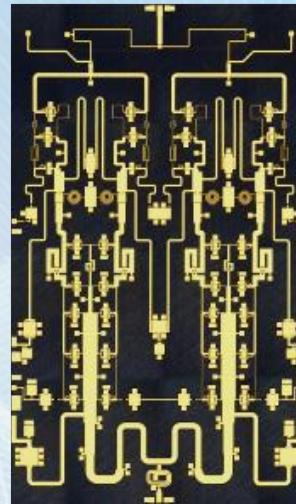


[12] 10W 2-20 GHz

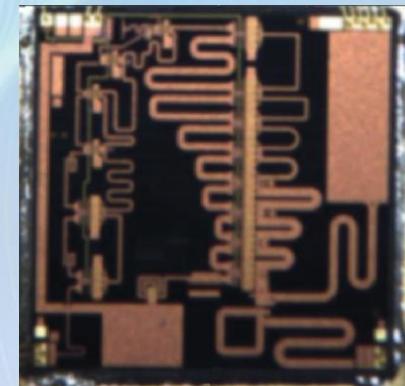

[13] 20W 2-20 GHz

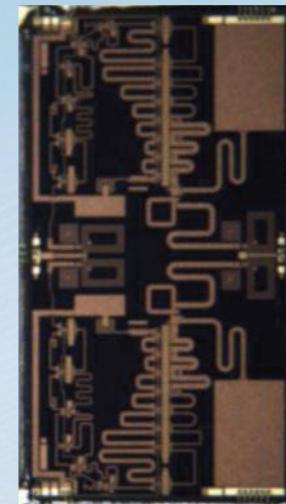


[14] 7-16W 16-40 GHz

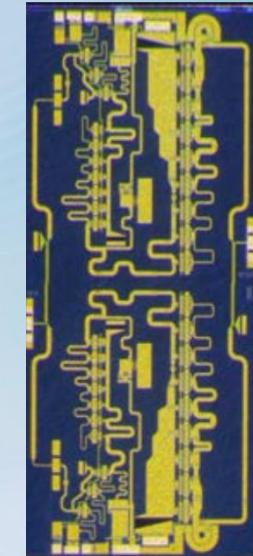


Other Topologies

Push Pull

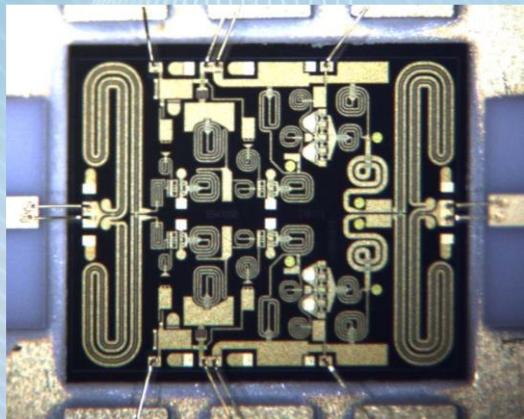


[15] 2W 6-12 GHz

Doherty

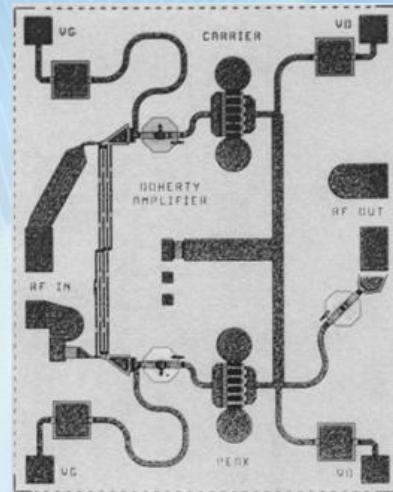

[16] 25dBm 17 GHz


Serially Combined

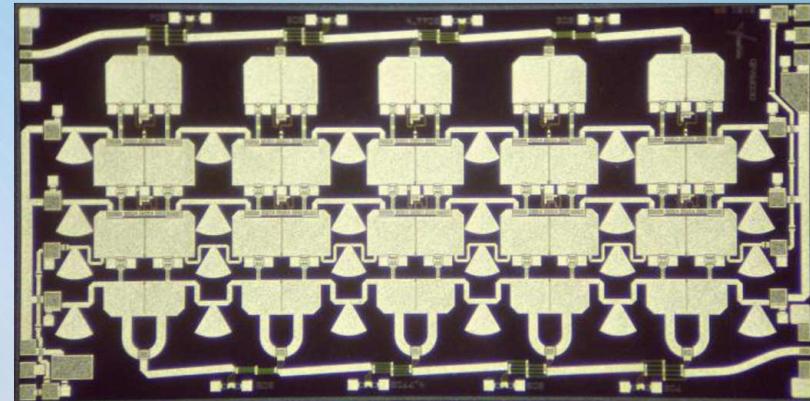

[17] 2W 75-100 GHz


Other Topologies

Load Modulated
Balanced Amplifier (LMBA)

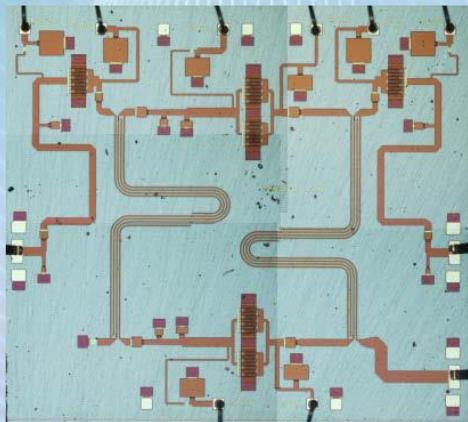


[18] 14W 8-9 GHz

Outphasing

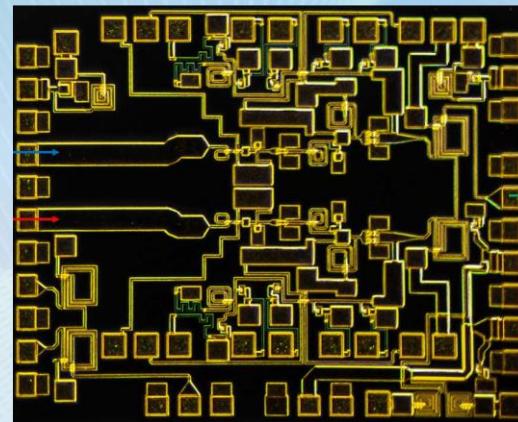

[19] 0.2W 18-38 GHz


Harmonic Injection

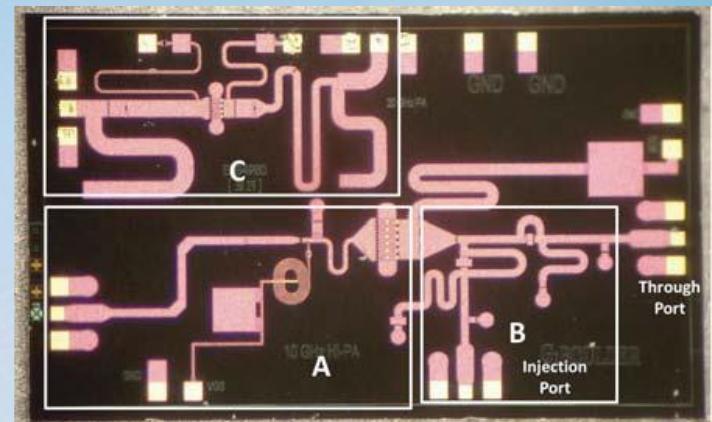

[20] 4W 10 GHz


Not a complete list of topologies by any means!

Preventing Pain: Avoiding The Pitfalls

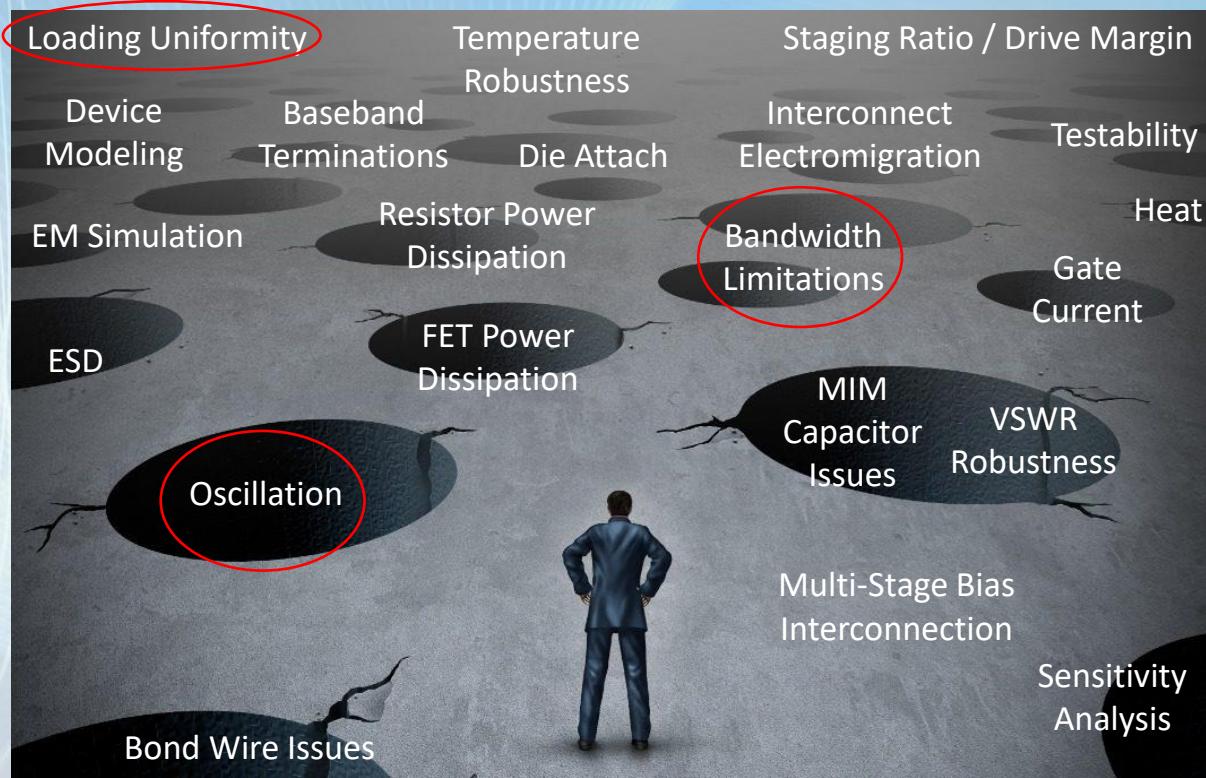

Understanding Bandwidth Limitations

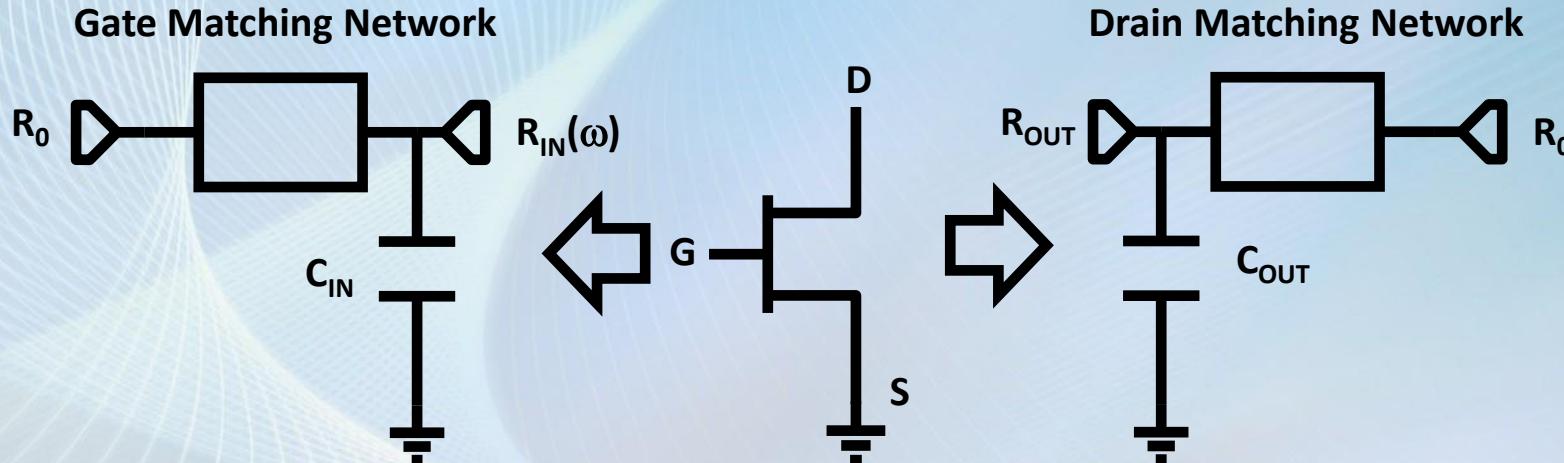- Input & output match targets are $\sim R \parallel C$ networks, specified in $\Omega \cdot \text{mm}$ and pF/mm
- Output Example: **50 $\Omega \cdot \text{mm}$, 0.3 pF/mm (relatively constant vs. frequency)**




How does output matching target impact the matching bandwidth?

Bode Fano Limitation

- Bode-Fano limit for matching to a $R \parallel C$ network


$$\int_0^{\infty} \ln|1/\Gamma(\omega)| d\omega \leq \frac{\pi}{R_p C_p}$$

$$B_w < \frac{4.343}{R_p C_p RL(dB)}$$

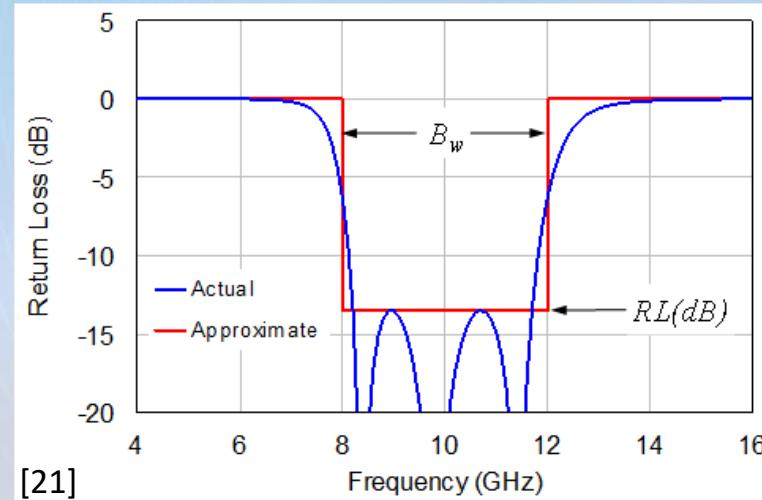

Let's investigate a 2-20 GHz design

Best Case Return Loss vs. Bandwidth

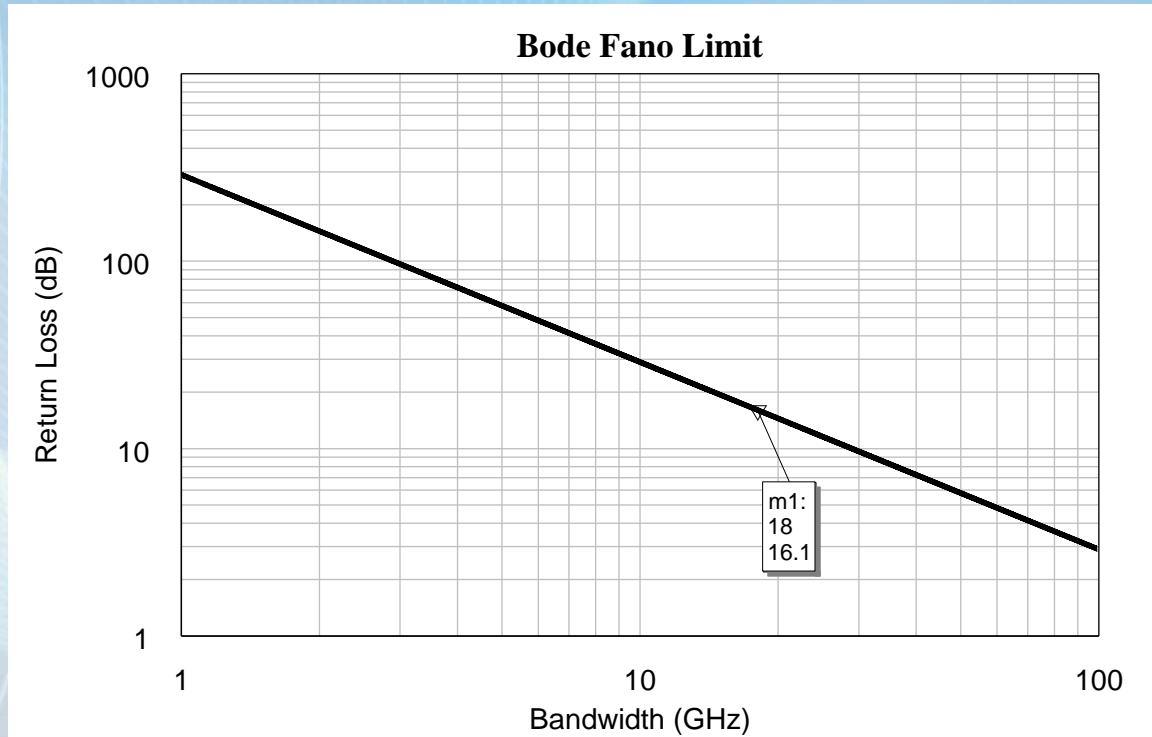

Output Example: **50 Ω·mm, 0.3 pF/mm**


Bode Fano Caveat

- Over a given bandwidth, I should be able to get the same match for any amount of FET periphery, right?

“One must keep in mind, however, that the network will, in general, involve an ideal transformer, since both the terminations are assumed to be one ohm. The turns ratio of the transformer can be determined easily from the zero frequency behavior of the network.” [22]


Example Reactive Matching Network

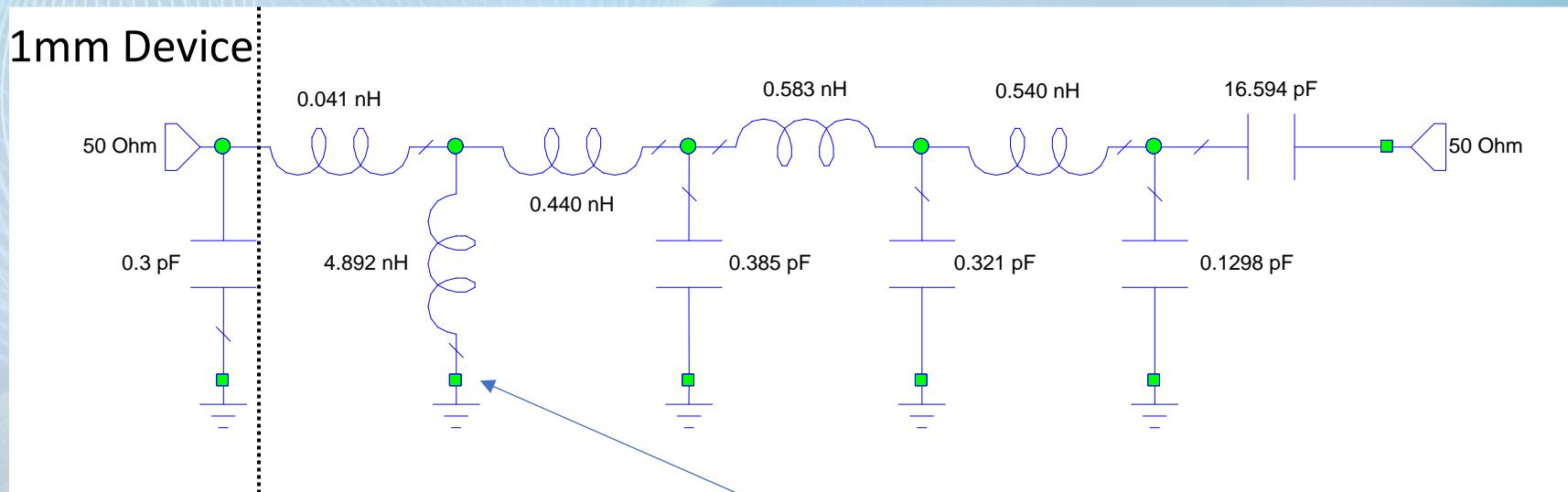- Example, network design, 2-20 GHz, 1mm of periphery




In practice, ground here is replaced with large bypass capacitor to apply drain voltage

Example Matching vs Frequency

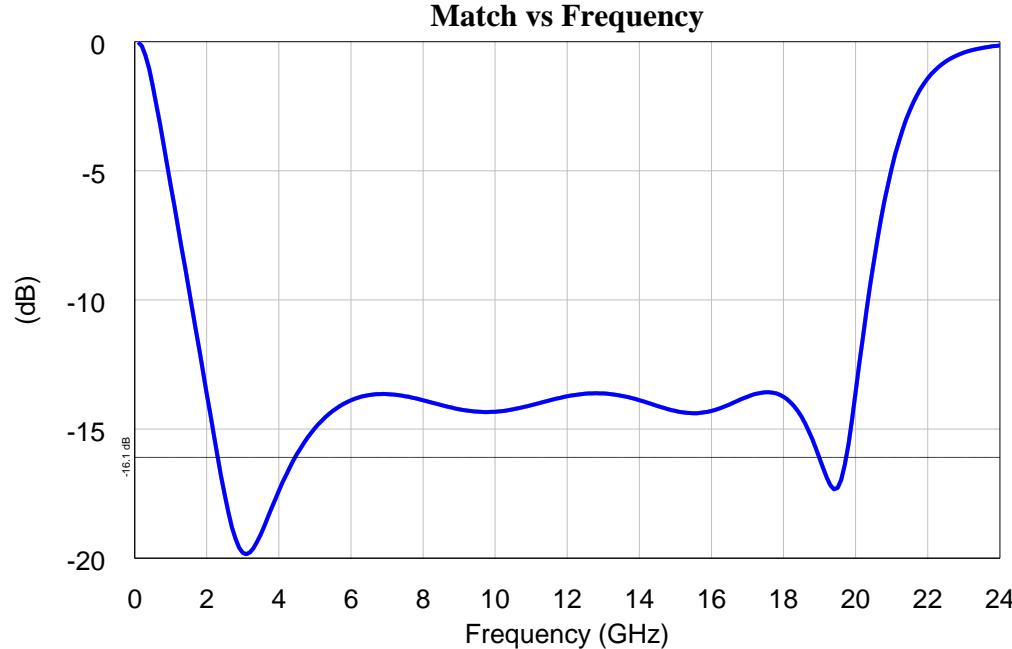


Network Scaling by Device Periphery

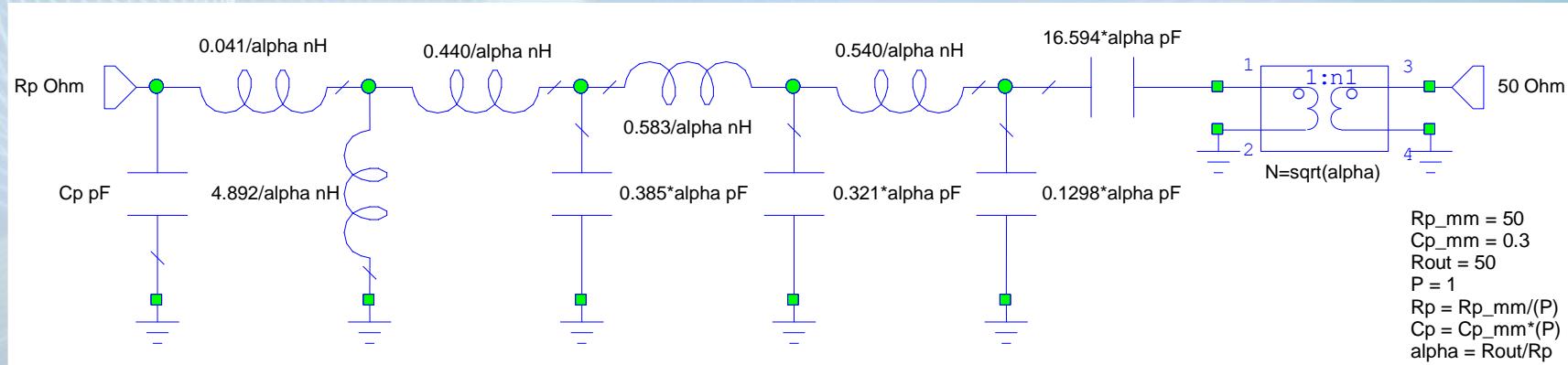- Network design with scaling and transformer, works for any amount of periphery (presuming you can realize the values and transformer)
- As periphery increases, inductors divide, capacitors multiply, and a transformer is required to match resistance




Practical Pitfall: No Transformer

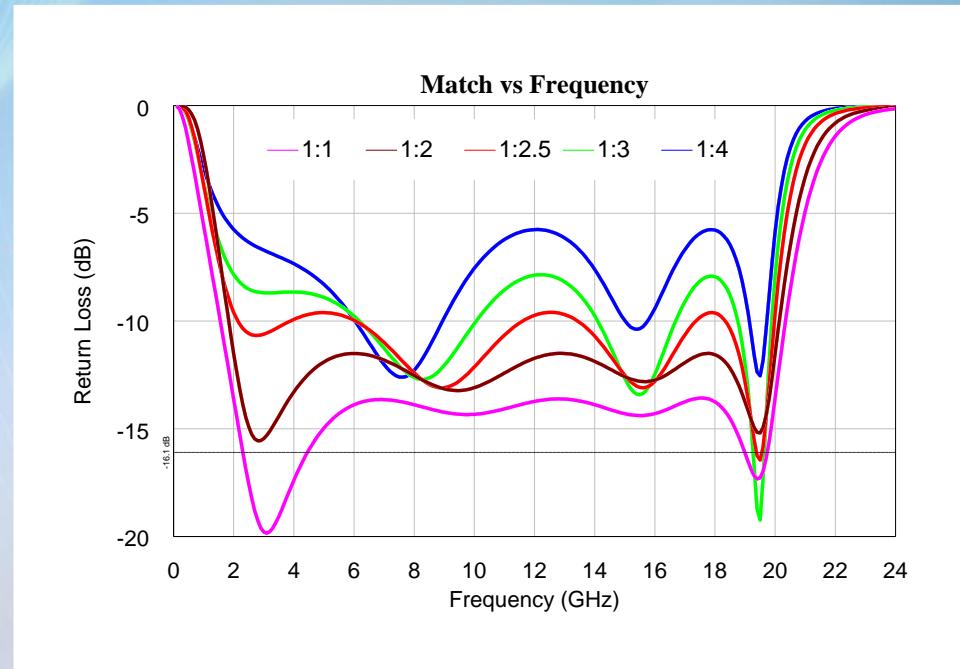- What happens if I don't use (have) a transformer?
- Network must be modified to do as "well as you can"
- Bandwidth degrades as R_p deviates from the output load
- But this doesn't affect my narrowband design... Not so fast!





Narrowband Example Performance

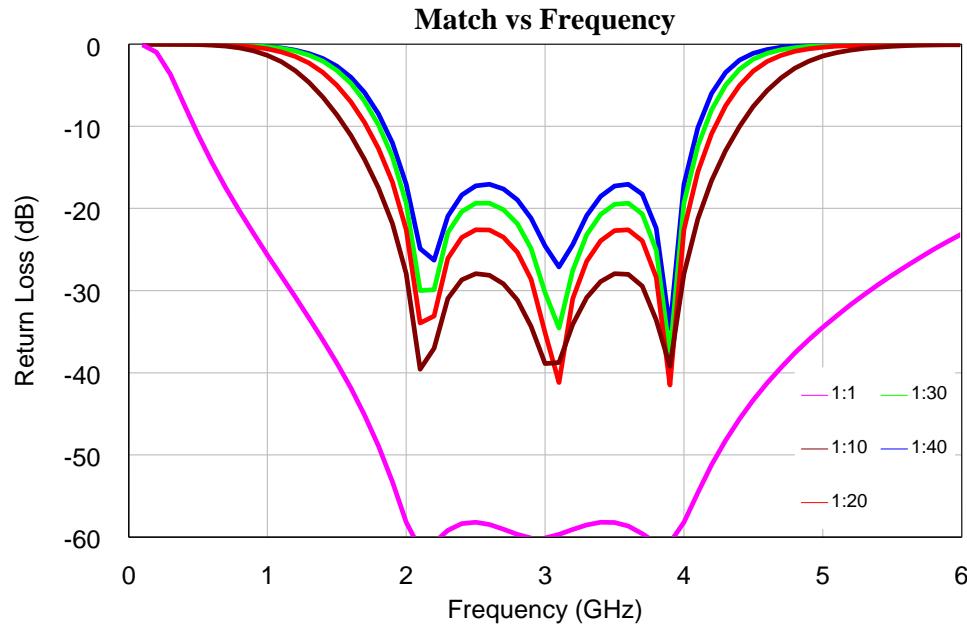

2-4 GHz Example, 1mm to 40mm Periphery

Trifilar Transformer Example (~1:2)

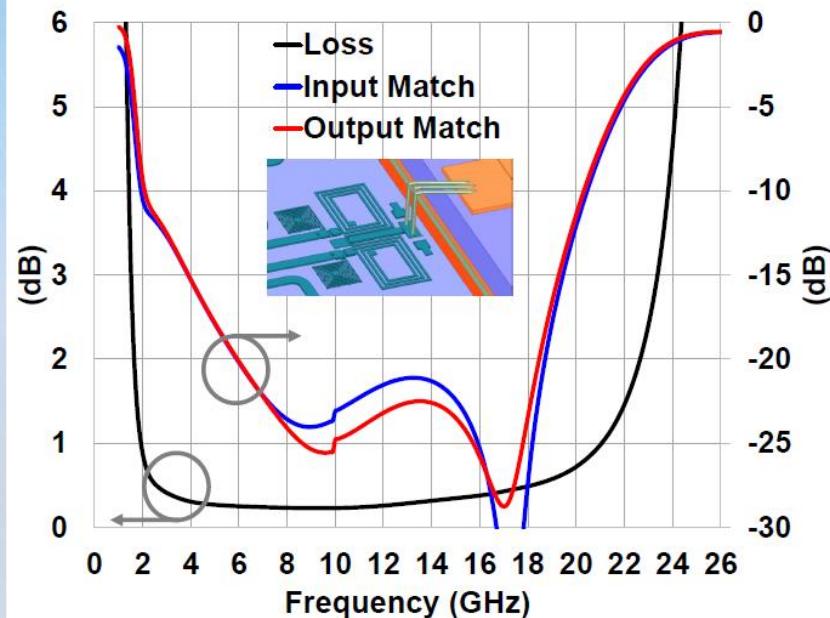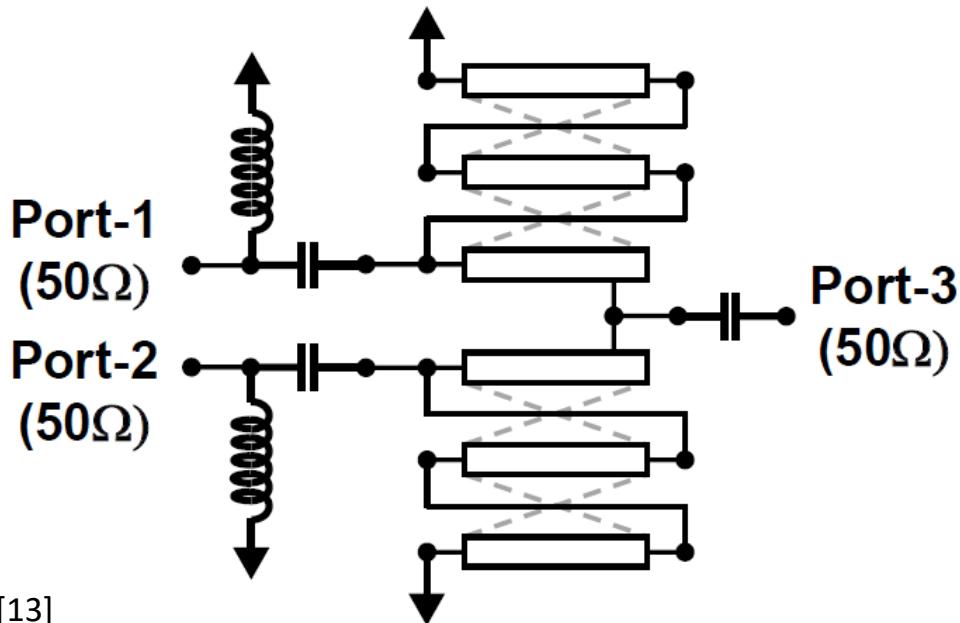


Summary

- Understand design limitations based on the chosen technology
- Transformers will enable you to come closer to the Bode-Fano limit
- Common broadband transformers include Ruthroff and Trifilar
- Narrowband transformers (e.g. quarter wave) often integrated into the matching network

Loading Asymmetry

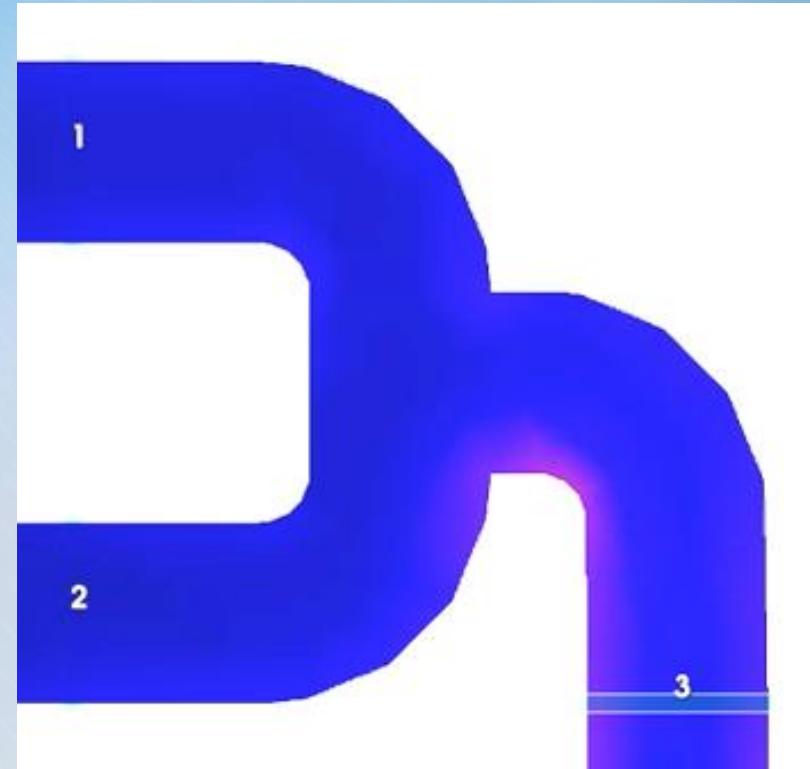- Port-1 and Port-2 are driven in-phase with equal power, Port-3 is terminated
- Current crowds around the bend, causing a difference in the loading at Port-1 vs. Port-2
- This would not show up with lumped element models of the bends and lines, EM Simulation is a must!



Efficient Power Combining


- Remember this from your microwave engineering class?

$$b = Sa$$

$$b = \begin{bmatrix} b_1 \\ \vdots \\ b_N \end{bmatrix} \quad a = \begin{bmatrix} a_1 \\ \vdots \\ a_N \end{bmatrix}$$

$$S = \begin{bmatrix} s_{11} & \cdots & s_{1N} \\ \vdots & \ddots & \vdots \\ s_{N1} & \cdots & s_{NN} \end{bmatrix}$$


Two Port Network Example

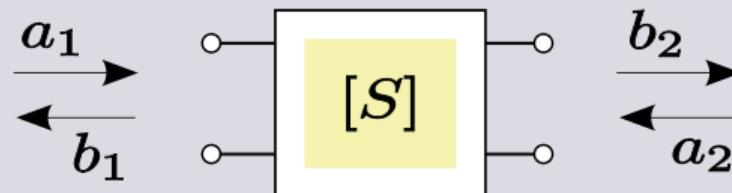

a_i = incident power wave at port- i
 b_i = reflected power wave at port- i
 S = Scattering Parameter Matrix

Efficient Power Combining

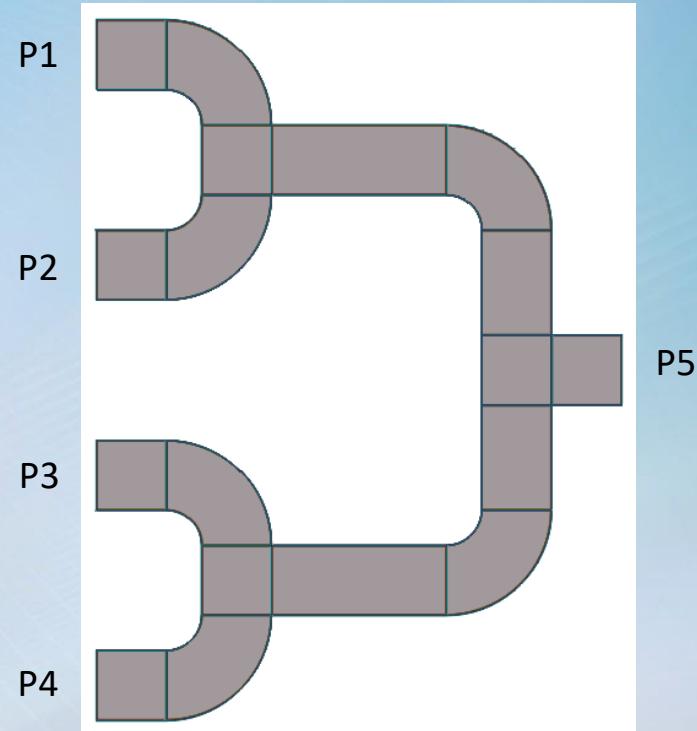- A greatly simplified 4-way combiner is shown on the right
 - Ports 1-4 are the input ports and port 5 is the output port
- To efficiently power combine, the input impedances at ports 1-4 need to be as uniform as possible
- What are the input impedances of this network at ports 1-4?
 - Hint: It's a function of the terminations and signals at all the ports



Efficient Power Combining

- Assume all incident power waves are equal (which implies driven port impedances are equivalent)


$$a_1 = a_2 = a_3 = a_4 = a_{inc}$$

- Assume no incident wave at the output port

$$a_5 = 0$$

- The equations simplify substantially
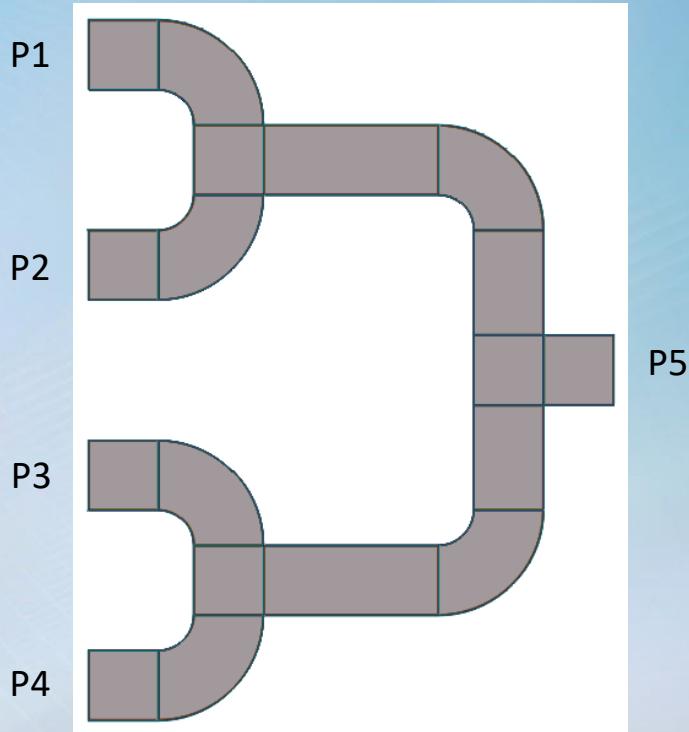
$$\begin{bmatrix} b_1 \\ b_2 \\ b_3 \\ b_4 \\ b_5 \end{bmatrix} = \begin{bmatrix} s_{11} + s_{12} + s_{13} + s_{14} \\ s_{21} + s_{22} + s_{23} + s_{24} \\ s_{31} + s_{32} + s_{33} + s_{34} \\ s_{41} + s_{42} + s_{43} + s_{44} \\ s_{51} + s_{52} + s_{53} + s_{54} \end{bmatrix} a_{inc}$$



Efficient Power Combining


- The effective reflection coefficients at ports 1-4 are evaluated by dividing by the incident wave a_{inc}

$$\begin{bmatrix} \Gamma_1 \\ \Gamma_2 \\ \Gamma_3 \\ \Gamma_4 \end{bmatrix} = \begin{bmatrix} b_1/a_{inc} \\ b_2/a_{inc} \\ b_3/a_{inc} \\ b_4/a_{inc} \end{bmatrix} = \begin{bmatrix} s_{11} + s_{12} + s_{13} + s_{14} \\ s_{21} + s_{22} + s_{23} + s_{24} \\ s_{31} + s_{32} + s_{33} + s_{34} \\ s_{41} + s_{42} + s_{43} + s_{44} \end{bmatrix}$$

- The input impedances are then easily evaluated

$$Z_i = \frac{Z_0^* + Z_0 \Gamma_i}{1 - \Gamma_i} \quad Z_0 = \text{Port Impedance}$$

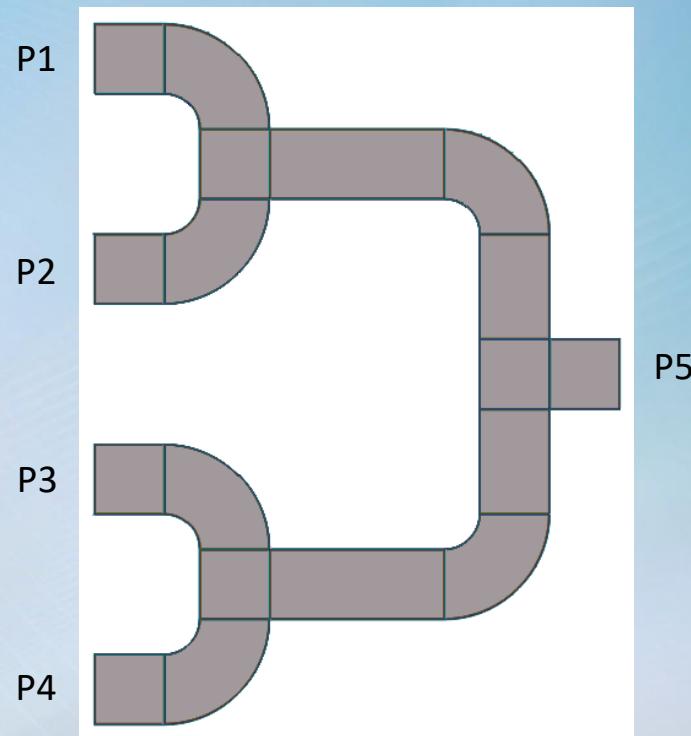- This equation is valid for complex port impedances



Efficient Power Combining


- Now we have a direct relationship between the S-parameters of the network and the load input impedance at the driven ports
- This impedance can be evaluated quickly in modern microwave circuit simulators
- A simple technique for evaluating power as a function of load is the Cripps Technique [24]
- In this technique the device has an optimum intrinsic load and maximum output power
- The device voltage or current limits when not optimally loaded, degrading the power
- This power estimate can now be calculated for each loaded FET and the balance can be optimized

P_{max}	= Maximum Power
R_{opt}	= Optimal Load (Resistive)
V_{max}	= Maximum Voltage
I_{max}	= Maximum Current
Z_L	= Load Impedance
Y_L	= Load Admittance
*	= Complex Conjugate

$$V_{max} = \sqrt{2P_{max}R_{opt}} \quad I_{max} = \sqrt{\frac{2P_{max}}{R_{opt}}}$$


$$P_{out} = \frac{1}{2} \min \left\{ \operatorname{Re} \left(I_{max}^2 Z_L \right), \operatorname{Re} \left(V_{max}^2 Y_L^* \right) \right\}$$

Example Schematic For Analysis

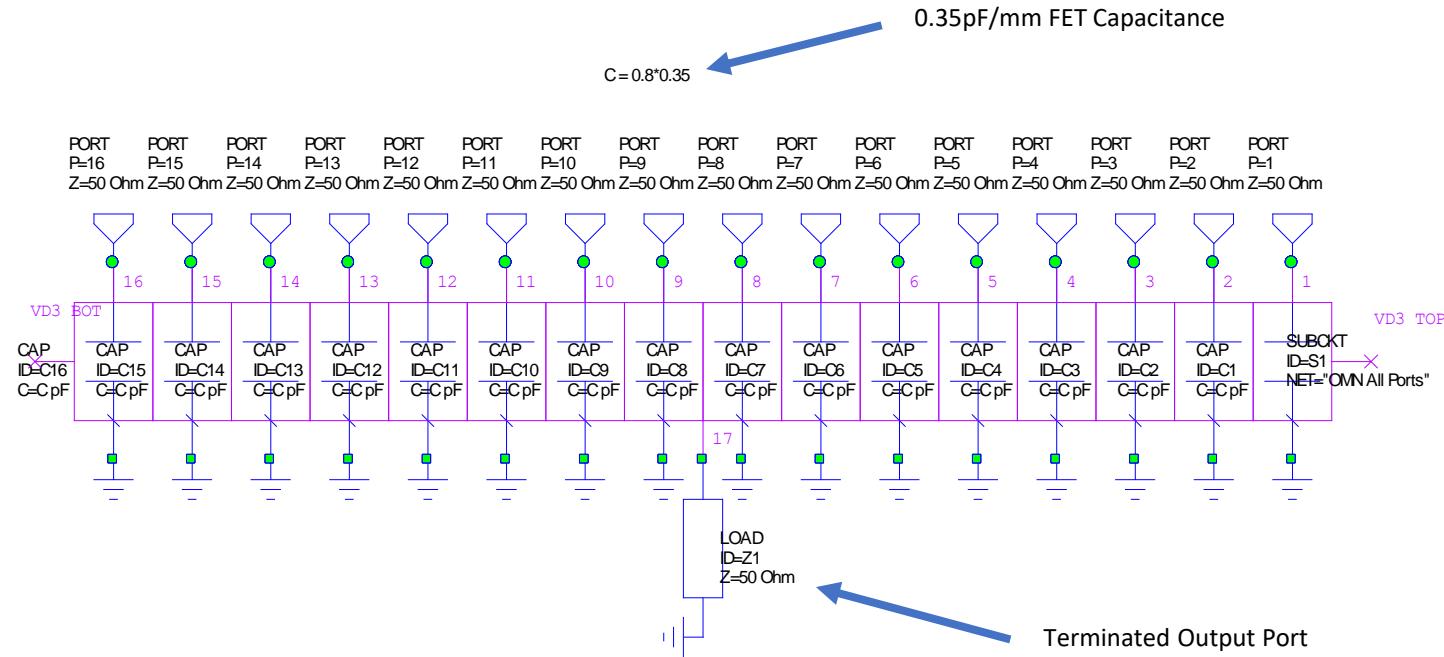


Intrinsic Loading

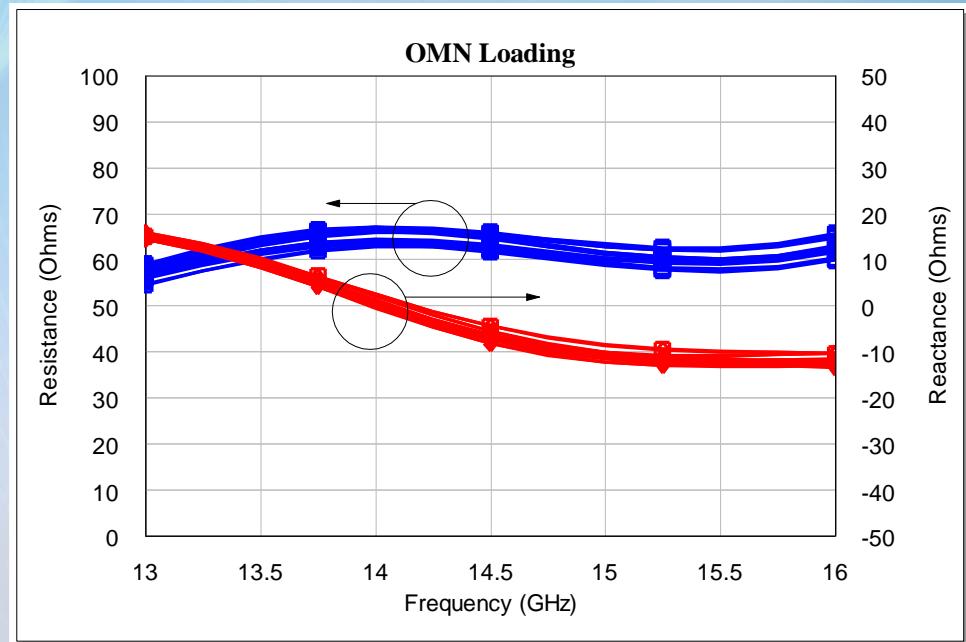- Impedance for all ports shows small variation
 - Resistance and reactance variation $\sim \pm 2.5\Omega$
- Variation is minimized by using physical layout asymmetries to improve electrical symmetry




Intrinsic Loading Impact on Cripps Power

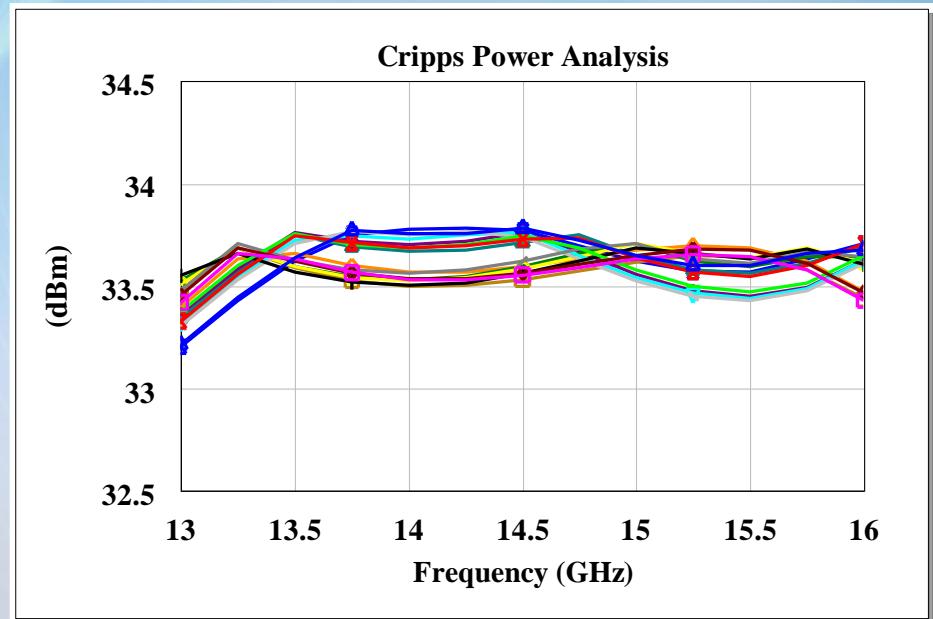- Analysis assumes maximum power of 33.8dBm / FET (3W/mm)
- Linear analysis of power balance shows less than 0.3dB variation in FET output power (in-band)
- In my experience, power balance is usually as good or better when analyzed with a non-linear model



Comparison with non-linear model analysis

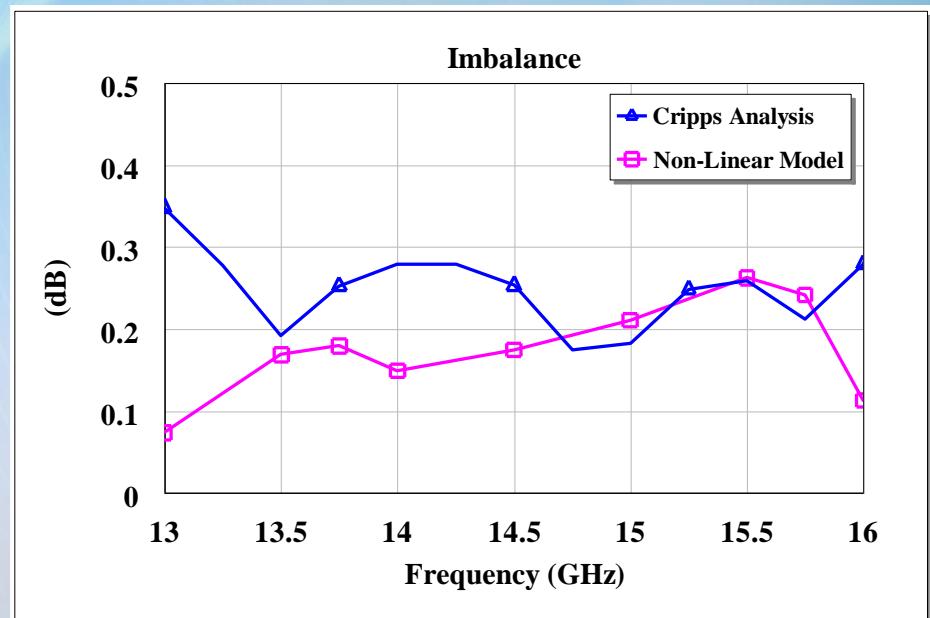- Analysis with non-linear model shows similar power balance
- So why use the linear analysis?
- Non-linear analysis takes ~2 minutes to converge (16 points)
- Linear analysis takes less than 1 second to converge
- Note: Apply same techniques to other amplifier stages, not just output stage



Summary

- Minimize load variation to maximize power combining efficiency
- Load variation and impact on output power can be analyzed with linear techniques
- Use physical asymmetry to enforce electrical symmetry


Preventing Oscillations

- Amplifier designers need stability analysis techniques during the design synthesis phase
- Rapid stability analysis techniques are highly desirable, which is why use of K-factor and mu-factor is so prevalent
- However, K-factor and mu-factor fail to reveal instabilities in multi-stage or parallel combined amplifiers

Preventing Oscillations


- Loop gain and Normalized determinant function (NDF) overcome the limitations of K-factor and mu-factor
- NDF and Stability Envelope fail to provide an indication of stability margin
- Loop gain provides an indication of stability margin, but requires additional odd mode loop analysis
- Both loop gain and NDF are slow analysis techniques which are not useful for design synthesis.

Standard Linear FET Model

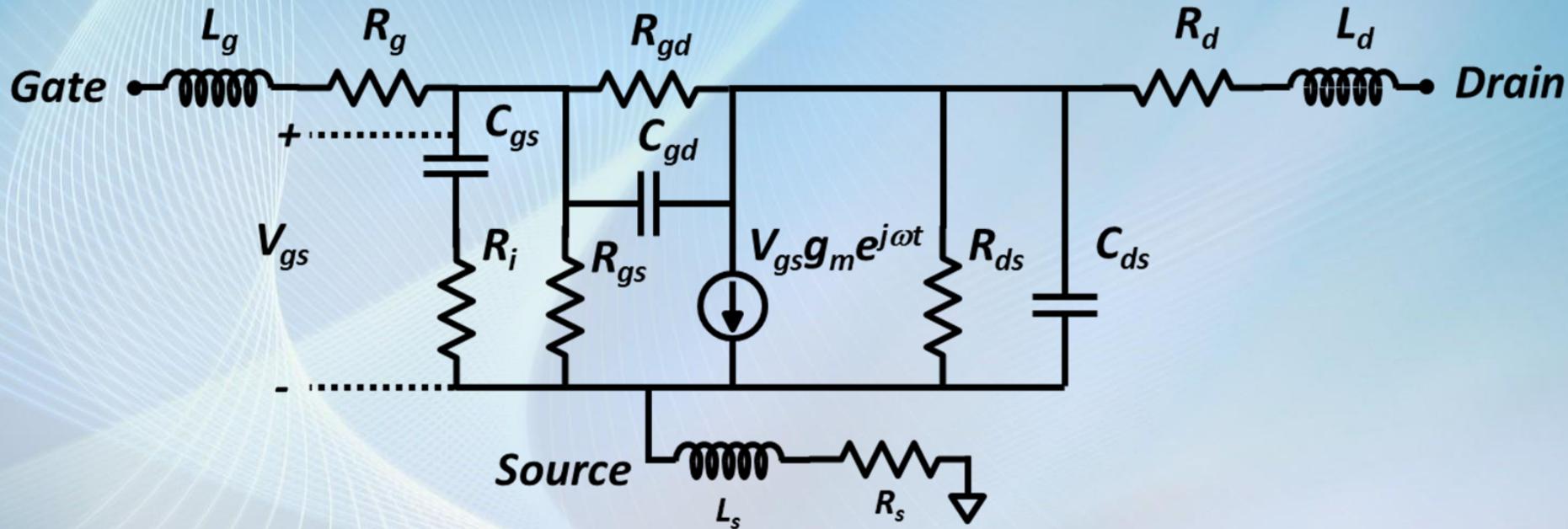


Loop Gain Stability Analysis Review

- Linear FET model typically used for loop gain evaluation
- Voltage gain from port-1 to port-2 is loop gain $G_{\text{loop}} = V_2 / V_1$
 - V_1 is injected at the device current source and resulting V_2 is measured at the intrinsic input to the device (V_{gs})
- Impedances at Gate and Drain impact G_{loop}
- Shorting port 1 to port 2 causes the model to degenerate to the standard linear FET model

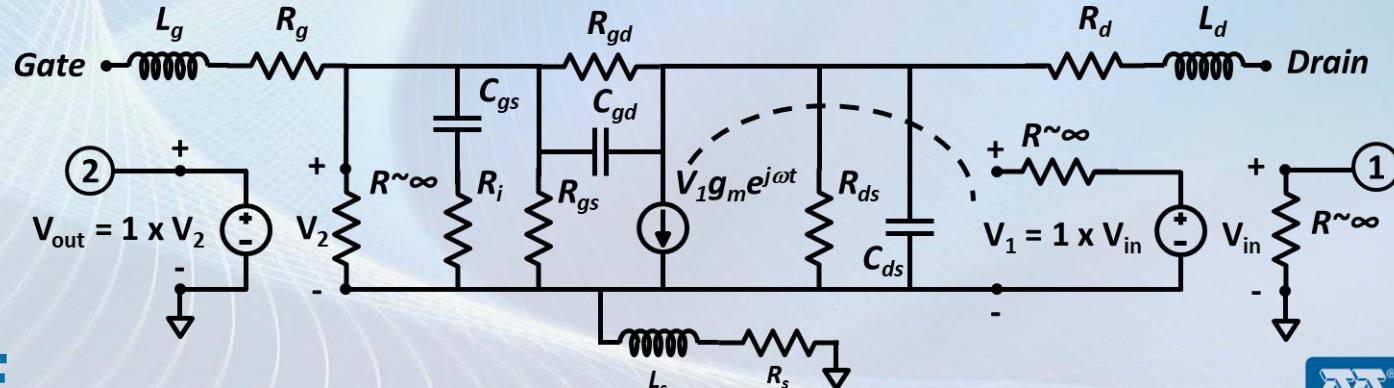

Loop Gain Stability Analysis Review

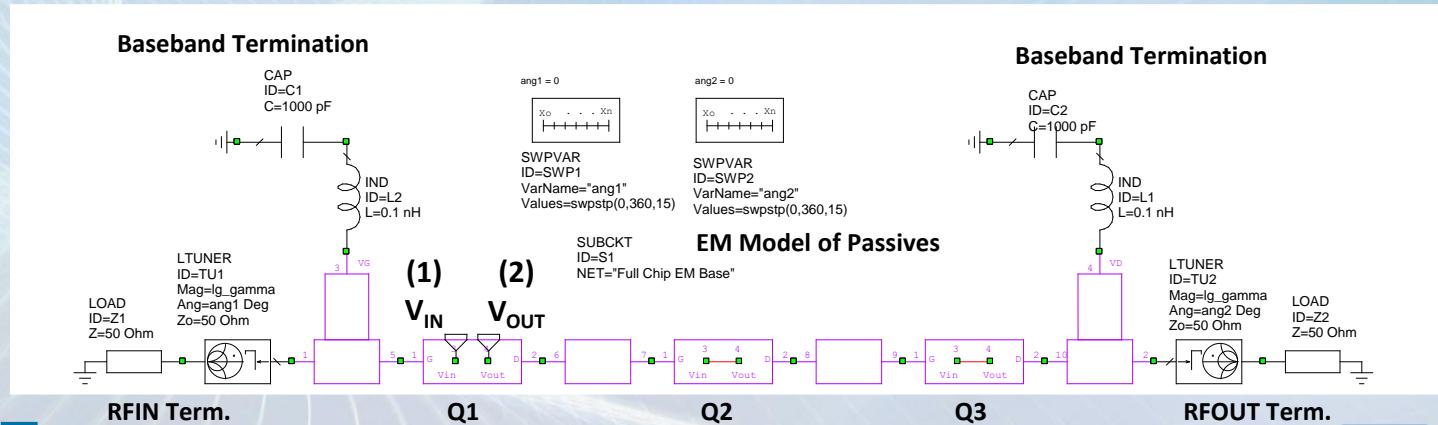
- Loop gain FET model is embedded in full PA
- RFIN and RFOUT terminations are swept, G_{Loop} is evaluated for each combination at each frequency
- Devices not under test have V_{in} and V_{out} shorted together
- Source not shown on device models below (grounded inside the subckt)



Loop Gain Stability Analysis Review

- At a specific frequency, for a fixed RFIN termination and varying RFOUT termination phase, the loop gain traces a circle in the complex plane
- Evaluating for a different fixed RFIN termination results in a different circle
- The collection of circles shows the loop gain behavior as a function of RFIN and RFOUT termination


Example loop gain circles and envelope

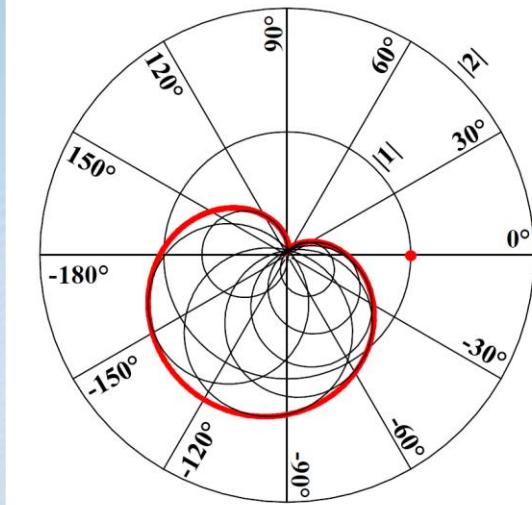

Motivation for Envelope Technique


- Designers don't particularly care about the circles themselves
- They care about the envelope of the circles, because that defines the phase margin
- Phase Margin: Minimum Phase where $|G_{loop}| \geq 1$
- Phase margin provides an indication of stability margin based on control theory, often 30° is acceptable
- Direct evaluation of the envelope would be highly desirable

Example loop gain circles and envelope

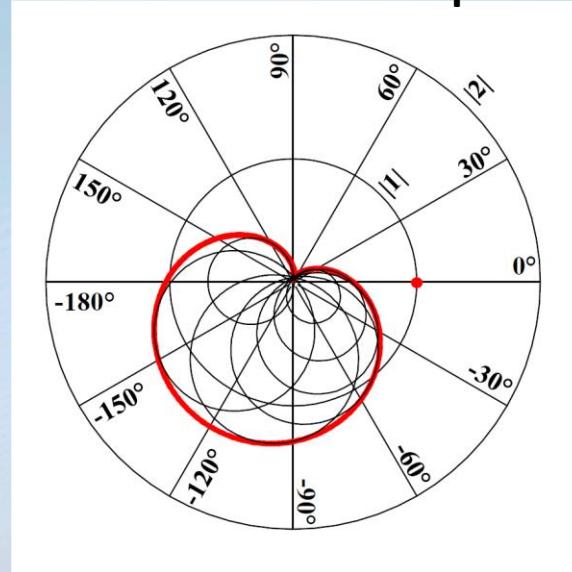

Loop Gain Envelope Derivation

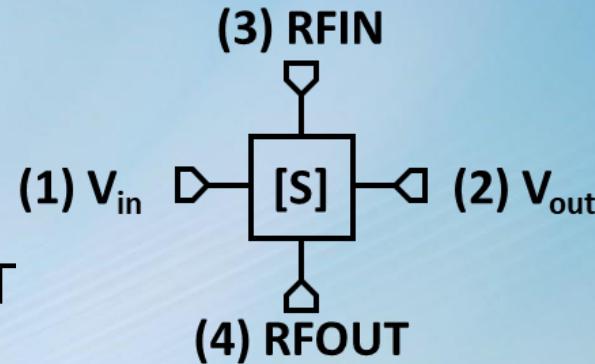- Consider the loop gain FET embedded in a MMIC amplifier, with simplified schematic shown to the right
- The loop gain ports (V_{in} , V_{out}), RFIN and RFOUT ports are interconnected by a 4-port network
- The 4-port S-parameters $[S]$ are reduced to 2-port S-parameters by applying the RFIN termination (Γ_s) and the RFOUT termination (Γ_L) mathematically



Loop Gain Envelope Equations [23]

- The loop gain is a function of the reduced 2-port S-parameter network

$$G_{Loop} = \frac{\bar{s}_{21}}{2}$$


- Lots of math allows the loop gain to be expressed as

$$G_{Loop} = \frac{c_1 \bar{\Gamma}_S + c_2 \bar{\Gamma}_L + c_3 \bar{\Gamma}_S \bar{\Gamma}_L + c_4}{d_1 \bar{\Gamma}_S + d_2 \bar{\Gamma}_L + d_3 \bar{\Gamma}_S \bar{\Gamma}_L + d_4}$$

Derivation

- The key takeaway is this mathematical form is identical to the NDF form, therefore the solution to the NDF stability envelope can be applied to loop gain to calculate the loop gain envelope
- Therefore, the loop gain envelope at a particular frequency is solved mathematically by evaluating the phase of Γ_L for each phase of Γ_S that results in a point on the envelope of all possible loop gains
- Furthermore, this is all now automated in Microwave Office!


Multi-stage MMIC PA Example

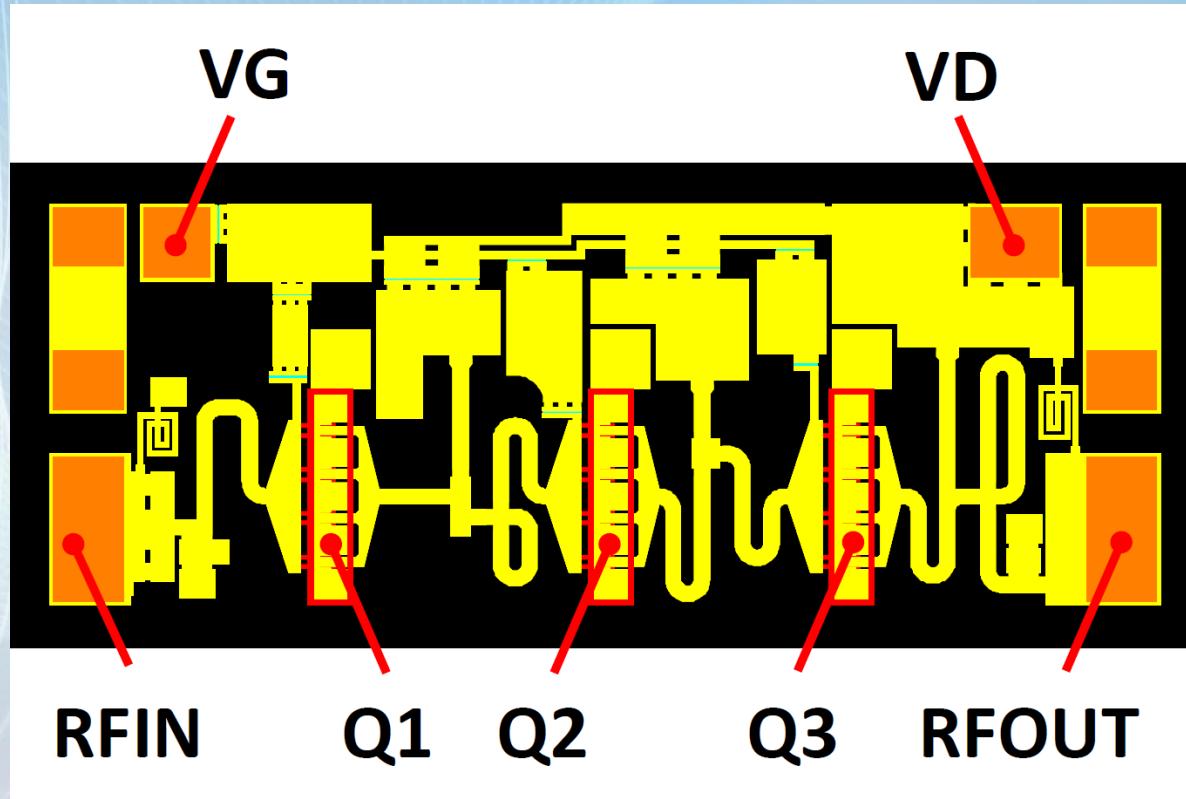

Multi-stage MMIC PA Example


- Loop gain circles shown in black, loop gain envelope shown in red
- Phase margin is minimum phase at which $|G_{\text{Loop}}| = 1$
- Phase margin $\sim 136^\circ$

38 GHz Loop Gain (Q1)

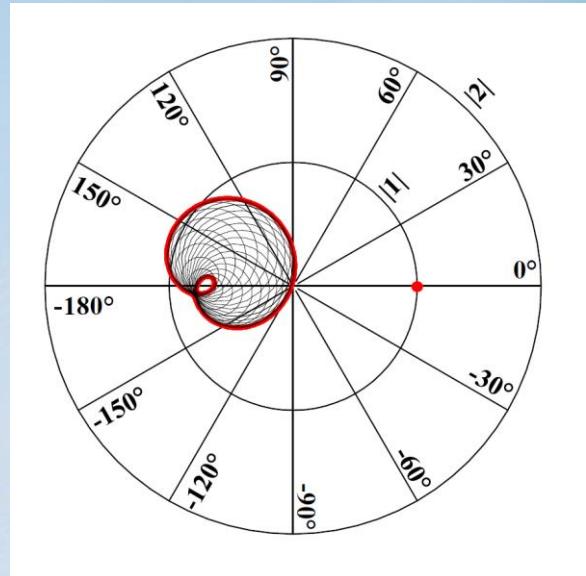

Phase Margin Evaluation

- Phase Margin can be easily evaluated in software from the loop gain envelope
- For a given frequency, find the minimum phase where $|G_{\text{Loop}}| \geq 1$. That is the phase margin.
- An example for Q1 vs. frequency is shown to the right
- AWR also has a gain margin measurement

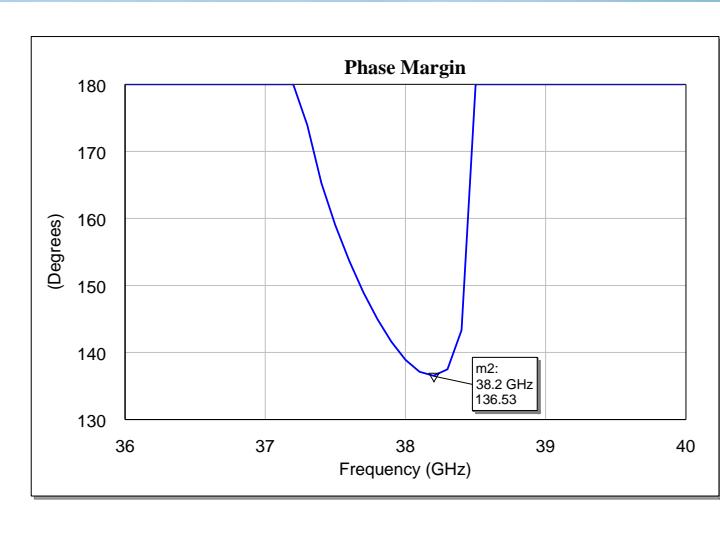

Analysis Speed Comparison

- 0.1 – 50 GHz, 0.1 GHz steps, 100 phase points, single device
- Traditional Loop Gain: **207.39 seconds**
- AWR Loop Gain Envelope: **0.7 seconds**
- 1000 phase points only increased LGE analysis time to **1.28 seconds**
- Analyzing all three devices with 1000 phase points only increased loop gain envelope analysis time to **3.11 seconds**! The traditional method would have taken well over **600 seconds** for only 100 phase points!

Summary

- Stability is critical, oscillation ruins your MMIC!
- Many techniques are available, Loop Gain Envelope is one useful for both synthesis and analysis of designs
- No matter which technique you use, make sure you understand the assumptions and limitations

Final Summary

- Compared GaAs vs. GaN, to assist technology selection
- Presented several common MMIC PA topologies
- Discussed bandwidth limitations, loading uniformity and stability analysis
- Go design a MMIC, it's a lot of fun! Always be looking to learn!

References

- [1] Hua Wang, Kyungsik Choi, Basem Abdelaziz, Mohamed Eleraky, Bryan Lin, Edward Liu, Yuqi Liu, Hossein Jalili, Mohsen Ghorbanpoor, Chenhao Chu, Tzu-Yuan Huang, Naga Sasikanth Mannem, Jeongsoo Park, Jeongseok Lee, David Munzer, Sensen Li, Fei Wang, Amr S. Ahmed, Christopher Snyder, Huy Thong Nguyen, and Michael Edward Duffy Smith, "Power Amplifiers Performance Survey 2000-Present," [Online]. Available: https://ideas.ethz.ch/Surveys/power_survey.html
- [2] A. P. de Hek, G. van der Bent and F. E. van Vliet, "400-Watt S-band Power Amplifier MMIC," *2021 16th European Microwave Integrated Circuits Conference (EuMIC)*, London, United Kingdom, 2022, pp. 160-163
- [3] K. Fukunaga, T. Sugitani, Y. Yamaguchi, D. Tsunami, M. Hangai and S. Shinjo, "X-band 100 W-class Broadband High Power Amplifier Using High Power Density GaN-HEMTs," *2020 IEEE International Symposium on Radio-Frequency Integration Technology (RFIT)*, Hiroshima, Japan, 2020, pp. 67-69
- [4] <https://www.qorvo.com/products/p/TGA2239>
- [5] S. Din, M. Wojtowicz and M. Siddiqui, "High power and high efficiency Ka band power amplifier," *2015 IEEE MTT-S International Microwave Symposium*, Phoenix, AZ, USA, 2015, pp. 1-4
- [6] J. Lange, "Interdigitated Strip-Line Quadrature Hybrid," *1969 G-MTT International Microwave Symposium*, Dallas, TX, USA, 1969, pp. 10-13, doi: 10.1109/GMTT.1969.1122649

References

- [7] D. F. Brown, P. Srivastava, K. Chu, W. Zhu, D. Dugas and M. Litchfield, "Millimeter Wave GaN MMIC Technologies for Next-gen Defense Applications," *2023 IEEE/MTT-S International Microwave Symposium - IMS 2023*, San Diego, CA, USA, 2023, pp. 101-104
- [8] M. Roberg, T. R. Mya Kywe, M. Irvine, O. Marrufo and S. Nayak, "40 W Ka-Band Single and Dual Output GaN MMIC Power Amplifiers on SiC," *2018 IEEE BiCMOS and Compound Semiconductor Integrated Circuits and Technology Symposium (BCICTS)*, San Diego, CA, USA, 2018, pp. 140-143
- [9] B. Cimbili, C. Friesicke, F. v. Raay, S. Wagner, M. Bao and R. Quay, "2.6- and 4-W E-Band GaN Power Amplifiers With a Peak Efficiency of 22% and 15.3%," in *IEEE Microwave and Wireless Technology Letters*, vol. 33, no. 6, pp. 847-850, June 2023
- [10] C. F. Campbell, M. D. Roberg, J. Fain and S. Nayak, "A 1–8GHz Gallium Nitride distributed power amplifier MMIC utilizing a trifilar transformer," *2016 11th European Microwave Integrated Circuits Conference (EuMIC)*, London, UK, 2016, pp. 217-220
- [11] M. Litchfield and A. Kingswood, "A 4–18 GHz, 35 W GaN MMIC Power Amplifier with Improved Thermal Performance," *2023 IEEE BiCMOS and Compound Semiconductor Integrated Circuits and Technology Symposium (BCICTS)*, Monterey, CA, USA, 2023, pp. 74-77
- [12] M. Roberg, M. Pilla, S. Schafer, T. R. Mya Kywe, R. Flynt and N. Chu, "A Compact 10W 2-20 GHz GaN MMIC Power Amplifier Using a Decade Bandwidth Output Impedance Transformer," *2020 IEEE/MTT-S International Microwave Symposium (IMS)*, Los Angeles, CA, USA, 2020, pp. 261-264
- [13] M. Roberg, M. Pilla, T. R. Mya Kywe, R. Flynt and N. Chu, "A 20W 2-20 GHz GaN MMIC Power Amplifier Using a Decade Bandwidth Transformer-Based Power Combiner," *2020 IEEE/MTT-S International Microwave Symposium (IMS)*, Los Angeles, CA, USA, 2020, pp. 1287-1290
- [14] C. F. Campbell, S. Nayak, Ming-Yih Kao and Shuoqi Chen, "Design and performance of 16–40GHz GaN distributed power amplifier MMICs utilizing an advanced 0.15 μ m GaN process," *2016 IEEE MTT-S International Microwave Symposium (IMS)*, San Francisco, CA, 2016, pp. 1-4

References

- [15] M. Roberg and B. Kim, "A 6-12 GHz Push-Pull GaN Amplifier for Low Harmonic Drive Applications," *2014 IEEE Compound Semiconductor Integrated Circuit Symposium (CS/ICS)*, La Jolla, CA, USA, 2014, pp. 1-4
- [16] C. F. Campbell, "A fully integrated Ku-band Doherty amplifier MMIC," in *IEEE Microwave and Guided Wave Letters*, vol. 9, no. 3, pp. 114-116, March 1999
- [17] J. M. Schellenberg, "A 2-W W-Band GaN Traveling-Wave Amplifier With 25-GHz Bandwidth," in *IEEE Transactions on Microwave Theory and Techniques*, vol. 63, no. 9, pp. 2833-2840, Sept. 2015
- [18] J. R. Powell, D. J. Shepphard, R. Quaglia and S. C. Cripps, "A Power Reconfigurable High-Efficiency X-Band Power Amplifier MMIC Using the Load Modulated Balanced Amplifier Technique," in *IEEE Microwave and Wireless Components Letters*, vol. 28, no. 6, pp. 527-529, June 2018
- [19] D. N. Martin, P. Enrico de Falco, M. Roberg, G. Lasser and T. W. Barton, "An 18–38-GHz K-/Ka-Band Reconfigurable Chireix Outphasing GaAs MMIC Power Amplifier," in *IEEE Transactions on Microwave Theory and Techniques*, vol. 68, no. 7, pp. 3028-3038, July 2020
- [20] A. Dani, M. Coffey and Z. Popovié, "4W X-band high efficiency MMIC PA with output harmonic injection," *2014 9th European Microwave Integrated Circuit Conference*, Rome, Italy, 2014

References

- [21] BCCTS 2019 MMIC PA Primer Course, M. Roberg & C. Campbell
- [22] R. M. Fano, "Theoretical Limitations on the Broadband Matching of Arbitrary Impedances," *Technical Report No. 41, Research Laboratory of Electronics, MIT*, 1948
- [23] M. Roberg, "Loop Gain Envelope Evaluation For Rapid MMIC Amplifier Stability Analysis," 2019 IEEE Texas Symposium on Wireless and Microwave Circuits and Systems (WMCS), Waco, TX, USA, 2019, pp. 1-4
- [24] S. C. Cripps, "A Theory for the Prediction of GaAs FET Load-Pull Power Contours," *1983 IEEE MTT-S International Microwave Symposium Digest*, Boston, MA, USA, 1983, pp. 221-223, doi: 10.1109/MWSYM.1983.1130864.